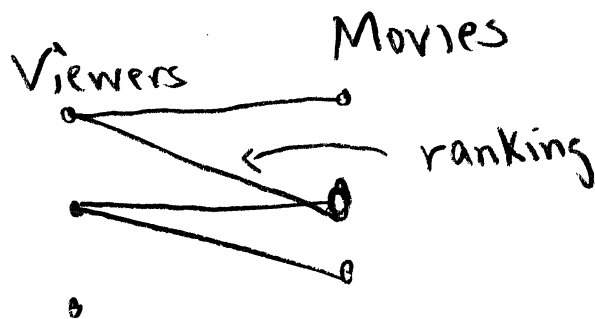


Resistive Model of a Graph & Random Walks

15-750
4/2/10

Motivation: Making a recommendation
(NETFLIX)



Question: Should we recommend M to V ?
 $\text{Score}(V, M)$

Idea 1 $\text{Score}(V, M) = \text{graph dist from } V \text{ to } M$

$$W_{ij} = \frac{1}{\text{rank}_{ij}}$$

$$\text{Score}(V, M) = \min_{V \rightarrow M} W(P)$$

Idea 2 $W(P) = \min_{e \in P} (\text{rank}(e))$

$$\text{Score}(V, M) \equiv \max_{V \rightarrow M} W(P)$$

Problem For 1) and 2) extra paths do not improve score

Idea 3 $\text{Score}(V, M) \equiv \text{Max flow from } V \text{ to } M.$

Problem Shorter paths do not improve score

Idea 4 View edges as conductors

$\text{Score}(V, M) = \text{effective conductance}$

Idea 5 Consider random walk from V to M


$\text{Score}(V, M) = \text{hit}(V, M) + \text{hit}(M, V)$

$\text{hit}(V, M) \equiv \text{Expect length random walk from } V, M$

We show 4) & 5) are related.

Resistance Theory

Ohms Law: $C \equiv$ conductance

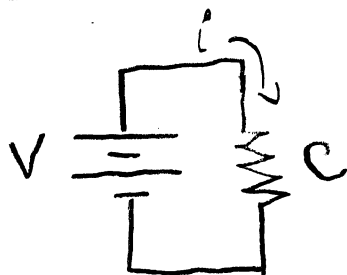

$R \equiv$ resistance


$V \equiv$ voltage

$i \equiv$ current

$$C = 1/R \quad i = C \cdot V = V/R$$

Facts no proof


Resistors in series

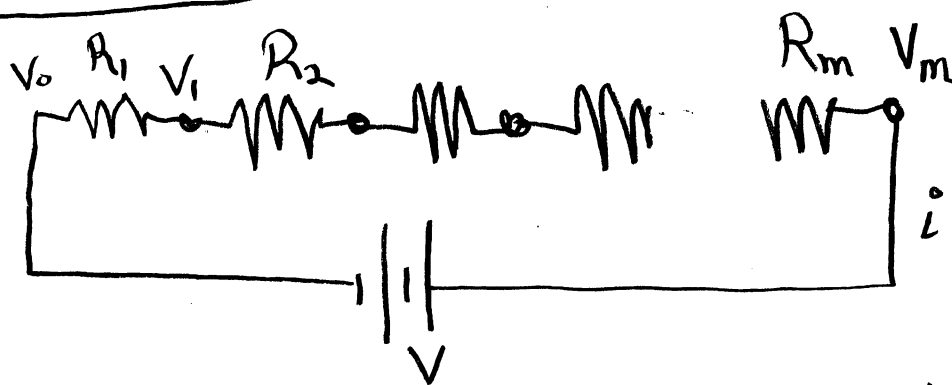

$$R = R_1 + \dots + R_m \quad C = \frac{1}{(1/C_1 + \dots + 1/C_m)} = ?$$

ie. $i = V/R$

Conductors in Parallel

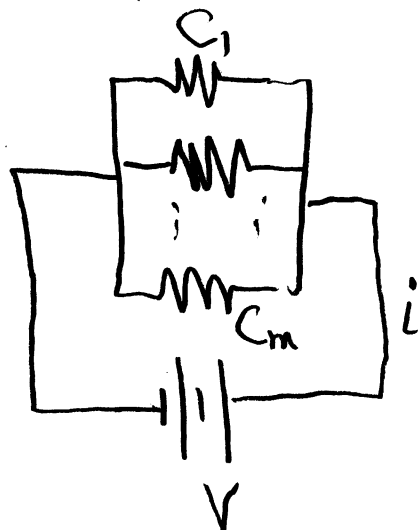


$$C = C_1 + \dots + C_m$$

$$ie \ i = V \cdot C$$

Effective Resistance/Conductance

Let G be a network of resistors

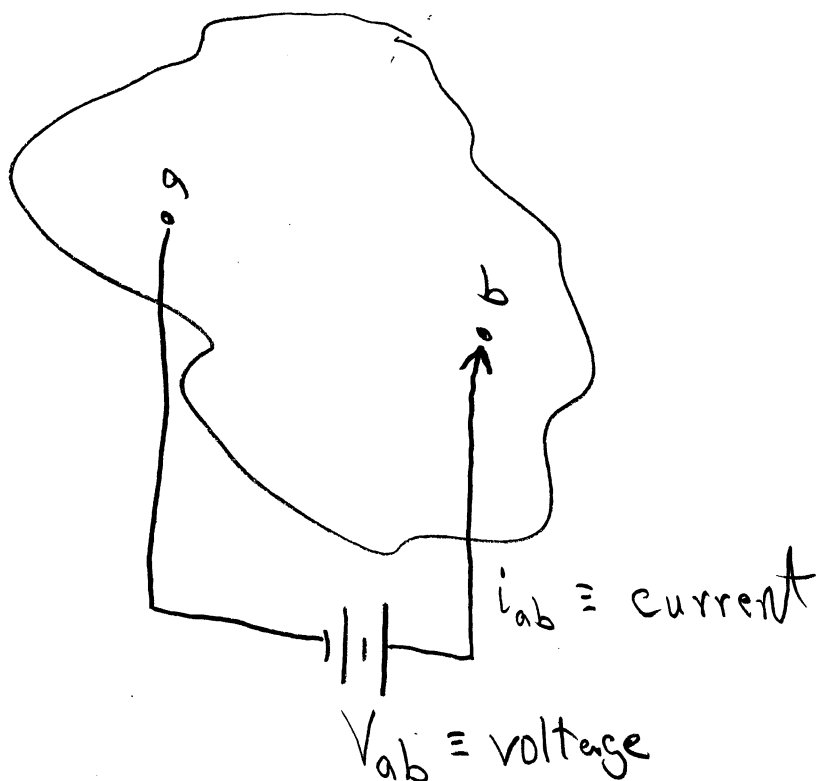

Def $R_{ab} = V_{ab} / i_{ab}$ $C_{ab} = 1 / R_{ab}$

HW) Show that R_{ab} is a metric space

ie 1) $R_{ab} \geq 0$

2) $R_{ab} = 0$ iff $a = b$


3) $R_{ab} = R_{ba}$

4) $R_{ac} \leq R_{ab} + R_{bc}$

Computing effective resistance

Use Kirchhoff's Law ie flow in = flow out

an example

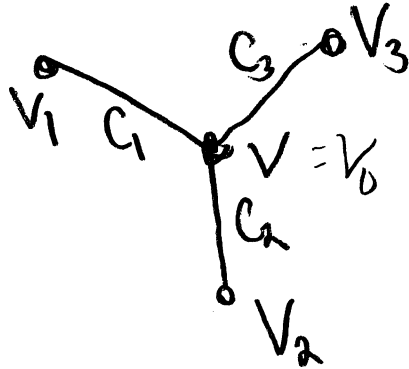

by Ohm's Law

$$i_1 = C_1(V - V_1)$$

$$i_2 = C_2(V - V_2)$$

$$i_3 = C_3(V - V_3)$$

$$\text{residual current} \equiv i_1 + i_2 + i_3$$

by Kirchhoff

$$i_1 + i_2 + i_3 = 0$$

$$C_1(V - V_1) + C_2(V - V_2) + C_3(V - V_3) = 0$$

$$(C_1 + C_2 + C_3)V = C_1V_1 + C_2V_2 + C_3V_3$$

$$C = C_1 + C_2 + C_3$$

$$CV = C_1 V_1 + C_2 V_2 + C_3 V_3$$

$$V = \frac{C_1}{C} V_1 + \frac{C_2}{C} V_2 + \frac{C_3}{C} V_3$$

V is convex combination of V_1, V_2, V_3

$$\text{residual current} = CV - C_1 V_1 - C_2 V_2 - C_3 V_3$$

The general case

$$G = (V, E, C) \quad C: E \rightarrow \mathbb{R}^+$$

$$V = \{V_1, \dots, V_n\}$$

$$d(V_i) = \sum_{(i,j) \in E} C_{ij}$$

$$A_{ij} = \begin{cases} C_{ij} & \text{if } (i,j) \in E \\ 0 & \text{o.w} \end{cases}$$

$$\text{Laplacian}(G) = L(G) = L$$

$$L_{ij} = \begin{cases} d(v_i) & \text{if } i=j \\ -C_{ij} & \text{if } (i,j) \in E \\ 0 & \text{o.w} \end{cases}$$

ie $L = D - A$ where $D = \begin{pmatrix} d(v_1) & & 0 \\ & \ddots & \\ 0 & & d(v_n) \end{pmatrix}$

Let V be a voltage setting of nodes

Note $(LV)_i = \text{residual current at } V_i$

Inverse: We inject currents and get voltages.

The net injected must be zero!

Goal: R_{in}

Method 1 solve
$$h \begin{pmatrix} 0 \\ V_2 \\ \vdots \\ V_{n-1} \\ 1 \end{pmatrix} = \begin{pmatrix} 0 \\ 1 \\ 0 \\ \vdots \\ 0 \\ -i \end{pmatrix} (*)$$

$$\tilde{V} = V/R$$

$$V = V_1, \dots, V_n$$

$$R = 1/i$$

return $1/i$

(*) is called a boundary valued prob.

In our case V_1 & V_n are the bdary

$(V_1, \dots, V_n)$ is called harmonic

because $V_i \in \text{interior} \Rightarrow$

V_i is convex combination of neighbors

Maximum Principle If f is harmonic
then min & max are on bdary

Pt $v \in \text{interior}$ then $\exists$ neig V_i & V_j st
 $V_i \leq v \leq V_j$

Uniqueness Principle If f & g are harmonic
with same bdary values then $f = g$

Pt $f - g$ is harmonic with zero on bdary

$$\Rightarrow f - g \equiv 0 \Rightarrow f = g$$



method 2 solve $LV = \begin{pmatrix} 1 \\ 0 \\ \vdots \\ 0 \\ -1 \end{pmatrix}$

Does V exist?

$$R_{1,n} = V_1 - V_n$$

Another way to view the Laplacian

Edge-vertex Matrix

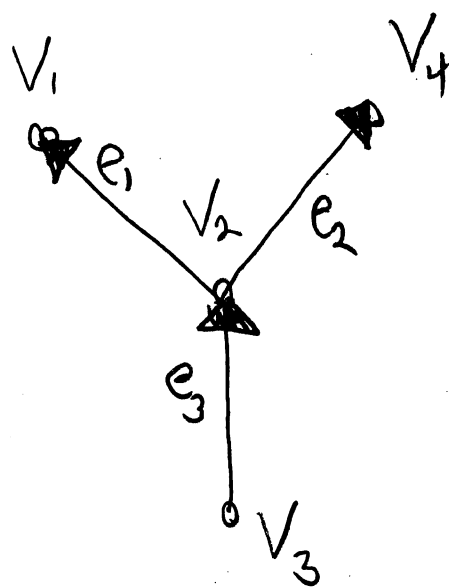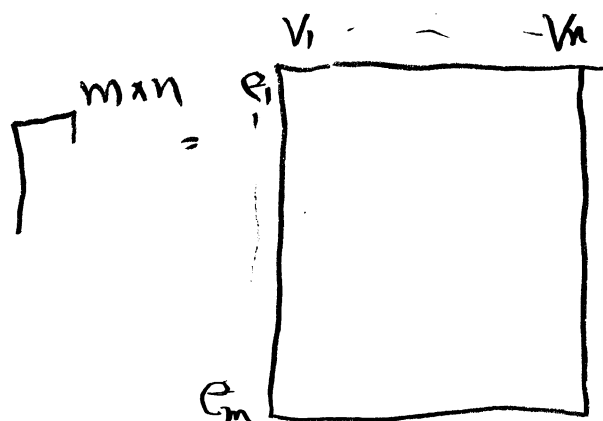

Orient each edge

$$\Gamma = \begin{array}{c|cccc} & v_1 & v_2 & v_3 & v_4 \\ \hline e_1 & 1 & -1 & 0 & 0 \\ e_2 & 0 & -1 & 0 & 1 \\ e_3 & 0 & 1 & -1 & 0 \end{array}$$

Let $C_1, \dots, C_m \equiv$ conductance of $e_1, \dots, e_m$


$$C = \begin{pmatrix} C_1 & & 0 \\ & \ddots & \\ 0 & & C_m \end{pmatrix}$$

Note $\Gamma V \equiv$ voltage drop across each edge
 $C \Gamma V \equiv$ current flow "

$\Gamma^T C \Gamma V \equiv$ residual current at each vertex

Thus $L = \Gamma^T C \Gamma$

Current & Energy/Power Dissipation

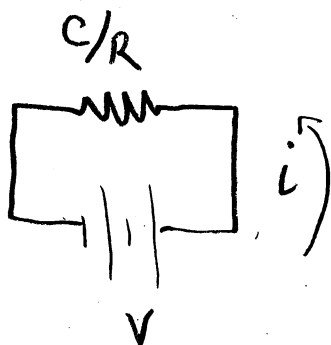

Newton Energy $\equiv$ Force $\cdot$ Distance
 $\equiv$ Volt $\cdot$ current

$$\begin{aligned} i &= CV \\ iR &= V \\ &\equiv V \cdot i \\ &\equiv CV^2 \\ &\equiv i^2 R \end{aligned}$$

Network $E = \frac{1}{2} \sum_{x,y} i_{xy} (V_x - V_y)$

$$\begin{aligned} V^T L V &= V^T \Gamma^T C \Gamma V = (\Gamma V)^T C (\Gamma V) \\ &= \sum_{\substack{\text{oriented} \\ (x,y) \in E}} C_{xy} (V_x - V_y)^2 = E \end{aligned}$$

Def $\dot{j}_x = \sum_y \dot{j}_{xy}$ (residual flow at x)

Let $W \equiv$ any voltage settings

$\dot{j} \equiv$ any flow from a to b

Conservation of Energy

$$(W_a - W_b) \dot{j}_a = \frac{1}{2} \sum_{x,y} (W_x - W_y) \dot{j}_{xy}$$

2RHS $\overset{\text{Pot}}{=} \sum_{x,y} (W_x - W_y) \dot{j}_{xy} = \sum_x W_x \sum_y \dot{j}_{xy} - \sum_y W_y \sum_x \dot{j}_{xy}$

$$= W_a \sum_y \dot{j}_{ay} + W_b \sum_y \dot{j}_{by}$$

$$- (W_a \sum_x \dot{j}_{xa} + W_b \sum_y \dot{j}_{yb})$$

$$= W_a \dot{j}_a + W_b \dot{j}_b - W_a (-\dot{j}_a) - W_b (-\dot{j}_b)$$

$$= W_a \dot{j}_a - W_b \dot{j}_a + W_a \dot{j}_a - W_b \dot{j}_a = 2(W_a - W_b) \dot{j}_a$$

Suppose $a, b \in V$ effective resistance R_{ab}

Effective energy $i_{ab}^2 R_{ab} = R_{ab}$ if $i_{ab} = 1$

Real energy using Kirchhoff's Law

Solve $LV = \begin{pmatrix} 1 \\ 0 \\ \vdots \\ -1 \end{pmatrix}$ $V_a = V_1$ $V_b = V_n$

$$\text{Energy} \equiv v^T L V = v^T \begin{pmatrix} 1 \\ 0 \\ \vdots \\ -1 \end{pmatrix} = V_a - V_b$$

Thm Real Kirchhoff energy $\equiv$ effective energy

Minimum Energy flow

Def (OR type flow)

$j: E \rightarrow \mathbb{R}$ is a flow from a to b if:

- 1) $j_{xy} = -j_{yx}$
- 2) $\sum_y j_{xy} = 0$ if $x \neq a, b$
- 3) $j_{xy} = 0$ $(x, y) \notin E$

Thomson's Principle

i is a unit Kirchhoff flow from a to b

j is any unit flow from a to b

$$\text{then } \sum i_{xy}^2 R_{xy} \leq \sum j_{xy}^2 R_{xy}$$

pf Let $d = j - i$ Then d is a zero flow ie $d_a = 0$

$$\sum j_{xy}^2 R_{xy} = \sum (i_{xy} + d_{xy})^2 R_{xy}$$

$$= \sum i_{xy}^2 R_{xy} + 2 \sum i_{xy} R_{xy} d_{xy} + \sum d_{xy}^2 R_{xy} \\ + 2 \sum (V_x - V_y) d_{xy} (*)$$

Set $W = V$ & $j = d$ then by conservation of energy

$$(*) \equiv 4(V_a - V_b) d_a = 0 \quad \text{thus}$$

$$\sum j_{xy}^2 R_{xy} = \sum i_{xy}^2 R_{xy} + \sum d_{xy}^2 R_{xy} \\ \geq \sum i_{xy}^2 R_{xy}$$

Rayleigh's Monotonicity Law

If $\forall xy \quad \bar{R}_{xy} \geq R_{xy}$ then $\bar{ER}_{ab} \geq ER_{ab}$

pt Let $j \equiv$ unit flow from a to b in $\bar{R}_x$
 $i \equiv$ " " " " R_x

$$\bar{ER}_{ab} = 1^2 \bar{ER}_{ab} = \frac{1}{2} \sum j_{xy}^2 \bar{R}_{xy}$$

$$\geq \frac{1}{2} \sum j_{xy}^2 R_{xy}$$

$$\geq \frac{1}{2} \sum i_{xy}^2 R_{xy} \quad (\text{Thomson})$$

$$= ER_{ab}$$