

# Random Walks on Graphs

15-750

4/5/10

Graph  $G = (V, E, w)$  (possibly directed)

$$w: E \rightarrow \mathbb{R}^+$$

$$w_i = w(V_i) = \sum_{(i,j) \in E} w_{ij} \quad P_{ij} = w_{ij} / w_i$$

---

Random walk on  $G$

Suppose, at a given time, we are at  $V_i \in V$ .

We move to  $V_j$  with probability  $P_{ij}$

---

eg.  $V \equiv$  all permutations of a deck of cards

$P_{ij} \equiv$  prop of going from  $\text{perm}_i$  to  $\text{perm}_j$  in one shuffle.

? Why do professional players play from a deck after 5 shuffles?

## Important Parameters

Access time or Hitting time

$H_{ij} \equiv$  Expected time to visit  $j$  starting at  $i$

Commute Time

$$K(i, j) = H(i, j) + H(j, i)$$

Cover Time

Expected time to visit all nodes  
max over all starting nodes

Mixing Rate (not covered)


## Random walks - the Symmetric Case

Do a random walk on a network of conductors!

Input:  $G = (V, E, C)$   $C_{ij} = C_{ji}$   $a, b \in V$

Consider a random walk starting at  $x$  and ending at  $b$ .

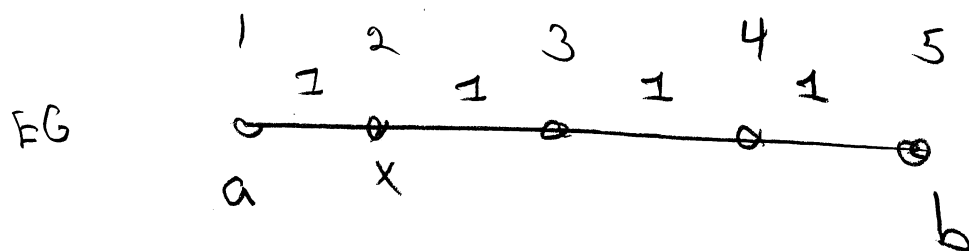Def  $h_x \equiv$  prob we visit  $a$  before visiting  $b$ .  
 $a \neq b$  starting from  $x$ .




$$h_a = 1 \quad h_b = 0$$

$$h_2?$$

$$h_2 > \frac{1}{2} \text{ why?}$$

$$h_a = 1 \text{ \& } h_b = 0$$

Suppose  $x \neq a, b$

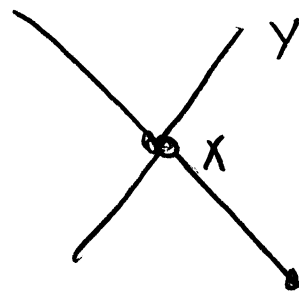

Claim 
$$h_x = \sum_y P_{xy} h_y$$

$$P_{xy} \geq 0 \quad \sum_y P_{xy} = 1$$

$h_x$  is a convex combination of its neighbors!

$h$  is harmonic with boundary  $a, b$ !


Lets solve the electrical prob

$V_a = 1$  &  $V_b = 0$  and  $x \neq a, b$  float.

$$x \neq a, b \quad V_x = \sum_y \frac{C_{xy}}{C_x} V_y \text{ but } \frac{C_{xy}}{C_x} = P_{xy}!$$

$$\Rightarrow h = V$$

Thm  $V_a = 1$  &  $V_b = 0$  then  $V_x = \text{prob visit } a \text{ before } b.$

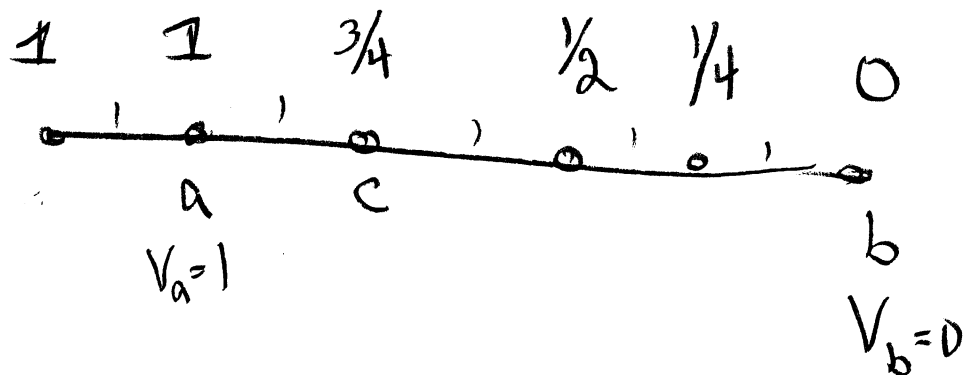
EG

$$h_c = 3/4$$

What does it mean (in random walks)

If we set  $V_{a_1} = V_{a_2} = 1$  &  $V_{b_1} = V_{b_2} = 0$

$X \neq a_1, a_2, b_1, b_2$  float?

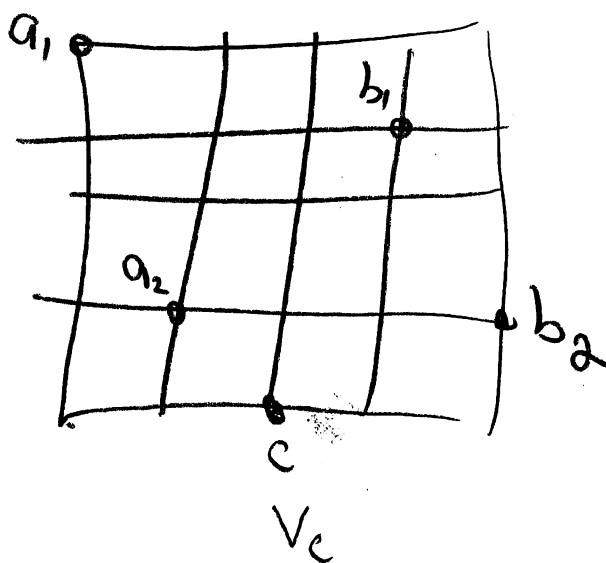

?

# Interpretation of Current

Assume  $G = (V, E, c)$   $a, b \in V$

Consider 1 unit of current flow from  $a$  to  $b$ ,

Say  $i$

What does  $i_{xy}$  correspond to in random walks?

---

Thm  $i_{xy}$  = Expected net # of traversals of  $E_{xy}$   
in random walk from  $a$  to  $b$ .

pf Slides 7, 8, 8A

Lets start with:

$U_x \equiv$  Expected number of visits to  $x$  before reaching  $b$  starting at  $a$ .

$$U_b = 0 \quad x \neq b$$

$$U_x = \sum_y U_y P_{yx} \quad \text{note } \sum_y P_{yx} \neq 1$$

$$\text{Recall } C_x = \sum_y C_{xy}$$

$$\text{note } C_x P_{xy} = C_x \left( \frac{C_{xy}}{C_x} \right) = C_{xy} = C_{yx} = C_y \left( \frac{C_{yx}}{C_y} \right) = C_y P_{yx}$$

$$U_x = \sum_y U_y \frac{C_y P_{yx}}{C_y} = \sum_y U_y \left( \frac{P_{xy} C_x}{C_y} \right)$$

$$\frac{U_x}{C_x} = \sum_y P_{xy} \left( \frac{U_y}{C_y} \right)$$

8

Let  $V_x = \left( \frac{U_x}{C_x} \right)$  then

$$V_x = \sum_y P_{xy} V_y \quad V_x \text{ is harmonic!}$$

What is the b.dary!  $V_b = 0$

Suppose we knew  $u_a$   $V_a = u_a / C_a$

$\therefore V$  is a voltage where  $V_b = 0$  &  $V_a = u_a / C_a$

Let  $i_{xy}$  be its current

$$i_{xy} = (V_x - V_y) C_{xy} = \left( \frac{U_x}{C_x} - \frac{U_y}{C_y} \right) C_{xy}$$

$$= U_x \left( \frac{C_{xy}}{C_x} \right) - U_y \left( \frac{C_{yx}}{C_y} \right) = U_x P_{xy} - U_y P_{yx}$$

$U_x P_{xy} = \text{expected \# of traversals from } x \text{ to } y$

$$U_y P_{yx} = "$$

"y to x


$j_{xy} = \text{expected \# net } xy \text{ traversals}$

What is net current flow from a to b?

ie  $\sum_y j_{ay}$

This must be 1

This proves Thm

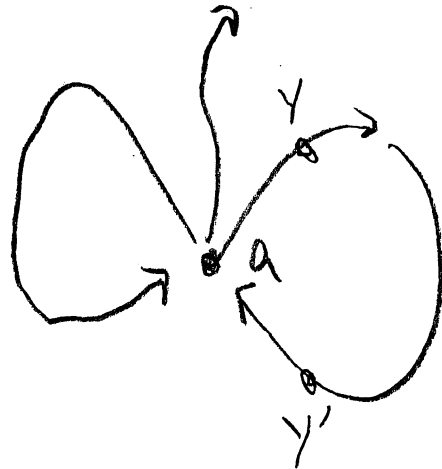

# How to compute hitting Time

Def  $h(x, b) \equiv$  expected time to reach  $b$  from  $x$

$$h_x = h(x, b) \quad b \text{ fixed}$$

Lets write a recurrence

$$h_b = 0 \quad x \neq b$$

(\*)

$$h_x = 1 + \sum_y h_y P_{xy}$$

How do we solve (\*)?

lets think of  $h_x$  as a voltage  $V_x$

$$V_b = 0 \quad V_x = 1 + \sum_y \frac{C_{xy}}{C_x} V_y$$

$$C_x V_x = C_x + \sum_y C_{xy} V_y$$

$$\underbrace{C_x V_x - \sum_y C_{xy} V_y}_{\text{Graph Laplacian}} = \underbrace{C_x}_{\text{residual current}}$$

Graph Laplacian

residual current

$$L V = \begin{pmatrix} c_1 \\ \vdots \\ c_{n-1} \\ \delta \end{pmatrix}$$

$V_n = 0$

$$c = \sum c_i$$

$$b = V_n$$

by conservation of flow

$$\delta = c_n - c$$

Alg for hitting time

$$\text{solve } L V = \begin{pmatrix} c_1 \\ \vdots \\ c_{n-1} \\ c_n - c \end{pmatrix}$$

$V_n = 0$

return  $V_x$

11

What about commute time?

$$a = v_1 \text{ \& \& } b = v_n$$

Solution 1

$$\text{solve } LV^b = \begin{pmatrix} c_n \\ \vdots \\ c_n - c \end{pmatrix} \quad LV^a = \begin{pmatrix} c_1 - c \\ \vdots \\ c_n \end{pmatrix}$$

$$h(1, n) = v_1^b - v_n^b$$

$$h(n, 1) = v_n^a - v_1^a$$

$$V = V^b - V^a$$

$$C(1, n) = (V^b - V^a)_1 - (V^b - V^a)_n$$

---

Solution 2

$$L(V^b - V^a) = LV^b - LV^a = \begin{pmatrix} 0 \\ \vdots \\ c_n - c \end{pmatrix} - \begin{pmatrix} c_1 - c \\ \vdots \\ c_n \end{pmatrix} = \begin{pmatrix} c \\ 0 \\ \vdots \\ 0 \\ -c \end{pmatrix} = c \begin{pmatrix} 1 \\ 0 \\ \vdots \\ 0 \\ -1 \end{pmatrix}$$

Solve  $LV = \begin{pmatrix} 1 \\ 0 \\ \vdots \\ -1 \end{pmatrix}$

return  $C(V, -V_n)$  but  $(V, -V_n) = R_{in}$

Thm  $C(a, b) = R_{ab} \cdot C$