

Random Walks on Graphs

Spectral
9/10/09

Graph $G = (V, E, w)$ (possibly directed)

$$w: E \rightarrow \mathbb{R}^+$$

$$w_i = w(v_i) = \sum_{(i,j) \in E} w_{ij} \quad P_{ij} = w_{ij} / w_i$$

Random walk on G

Suppose, at a given time, we are at $v_i \in V$.

We move to v_j with probability P_{ij}

EG $V \equiv$ all permutations of a deck of cards

$P_{ij} \equiv$ prop of going from perm _{i} to perm _{j} in one shuffle.

? Why do professional players play from a deck after 5 shuffles?

EG. $V \in$ All web pages

2

$P_{ij} \equiv$ prob of going from V_i to V_j in one click

? How does (prob of being at V_i) compare to (prob of being at V_j)

Questions:

- 1) Does \exists a steady state
- 2) How do we compute the prob of being at some node?
- 3) When are we close to the steady state

Important Parameters

Access time or Hitting time

$H_{ij} \equiv$ Expected time to visit j starting at i

Commutate Time

$$K(i, j) = H(i, j) + H(j, i)$$

Cover Time

Expected time to visit all nodes
max over all starting nodes

Mixing Rate (Todo)


Random walks - the Symmetric Case

Do a random walk on a network of conductors!

Input: $G = (V, E, C)$ $C_{ij} = C_{ji}$ $a, b \in V$

Consider a random walk starting at x and ending at b .

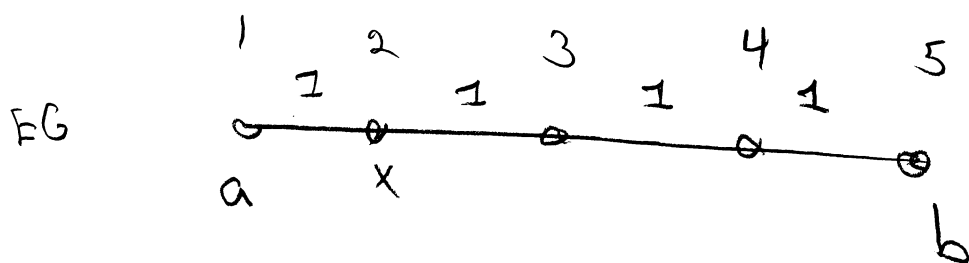Def $h_x \equiv$ prob we visit a before visiting b .
 $a \neq b$ starting from x .




$$h_a = 1 \quad h_b = 0$$

$$h_2 ?$$

$$h_2 > \frac{1}{2} \text{ why?}$$

$$h_a = 1 \text{ \& } h_b = 0$$

Suppose $x \neq a, b$

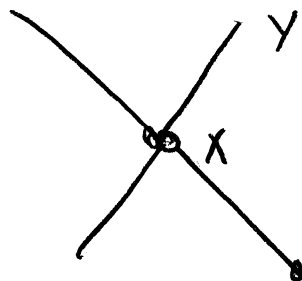

Claim
$$h_x = \sum_y P_{xy} h_y$$

$$P_{xy} \geq 0 \quad \sum_y P_{xy} = 1$$

h_x is a convex combination of its neighbors!

h is harmonic with boundary a, b !

Lets solve the electrical prob


$V_a = 1$ & $V_b = 0$ and $x \neq a, b$ float.

$$x \neq a, b \quad V_x = \sum_y \frac{C_{xy}}{C_x} V_y \quad \text{but} \quad \frac{C_{xy}}{C_x} = P_{xy}!$$

$$\Rightarrow h = V$$

Thm $V_a = 1$ & $V_b = 0$ then $V_x =$ prob visit a before b .

EG

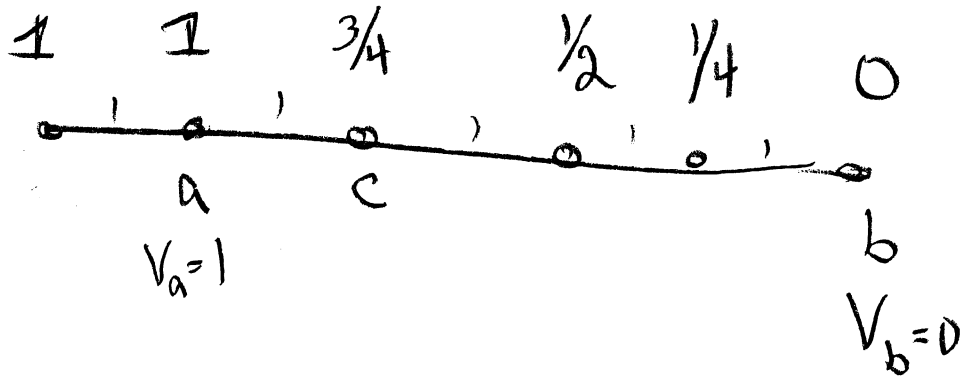


$$h_c = 3/4$$

What does it mean (in random walks)

if we set $V_{a_1} = V_{a_2} = 1$ & $V_{b_1} = V_{b_2} = 0$

$X \neq a_1, a_2, b_1, b_2$ float?

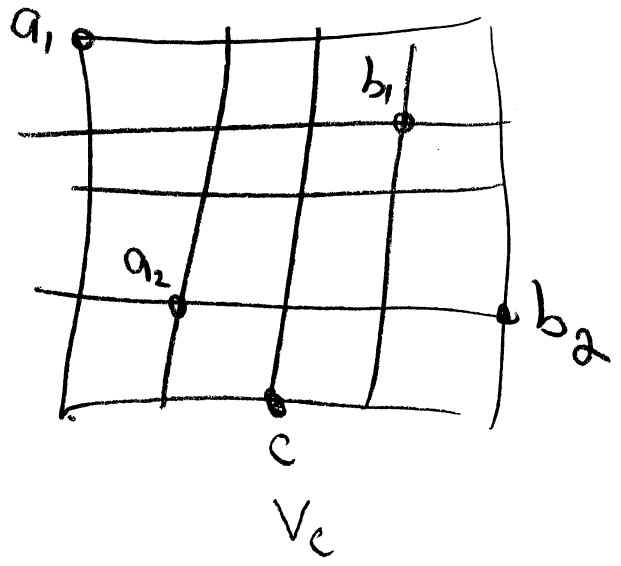

Interpretation of Current

Assume $G = (V, E, C)$ $a, b \in V$

Consider 1 unit of current flow from a to b ,

Say i

What does i_{xy} correspond to in random walks?

Thm $i_{xy} = \text{Expected net \# of traversals of } E_{xy}$
in random walk from a to b .

pf Slides 7, 8, 8A

Lets start with:

$U_x \equiv$ Expected number of visits to x before reaching b starting at a .

$$U_b = 0 \quad x \neq b$$

$$U_x = \sum_y U_y P_{yx} \quad \text{note } \sum_y P_{yx} \neq 1$$

$$\text{Recall } C_x = \sum_y C_{xy}$$

$$\text{note } C_x P_{xy} = C_x \left(\frac{C_{xy}}{C_x} \right) = C_{xy} = C_{yx} = C_y \left(\frac{C_{yx}}{C_y} \right) = C_y P_{yx}$$

$$U_x = \sum_y U_y \frac{C_y P_{yx}}{C_y} = \sum_y U_y \left(\frac{P_{xy} C_x}{C_y} \right)$$

$$\frac{U_x}{C_x} = \sum_y \hat{P}_{xy} \left(\frac{U_y}{C_y} \right)$$

$U_x P_{xy} =$ expected # of traversals from x to y

$U_y P_{yx} = "$


" y to x

$j_{xy} =$ expect # net xy traversals.

what is net current flow from a to b ?

ie $\sum_y j_{ay}$

This must be 1

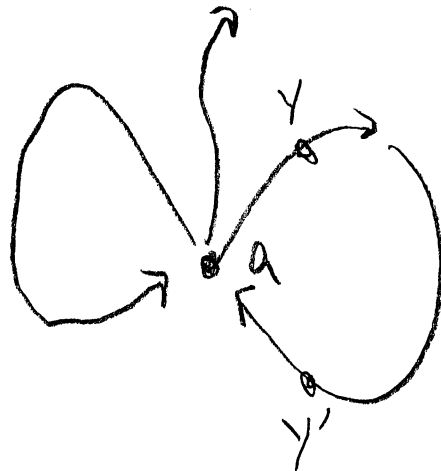

This proves Thm

8

Let $V_x = \left(\frac{U_x}{C_x} \right)$ then

$$V_x = \sum_y P_{xy} V_y \quad V_x \text{ is harmonic!}$$

What is the boundary! $V_b = 0$

Suppose we knew u_a $V_a = u_a / C_a$

$\therefore V$ is a voltage where $V_b = 0$ & $V_a = u_a / C_a$

Let i_{xy} be its current

$$i_{xy} = (V_x - V_y) C_{xy} = \left(\frac{U_x}{C_x} - \frac{U_y}{C_y} \right) C_{xy}$$

$$= U_x \left(\frac{C_{xy}}{C_x} \right) - U_y \left(\frac{C_{yx}}{C_y} \right) = U_x P_{xy} - U_y P_{yx}$$

How to compute hitting time

Def $h(x, b) \equiv$ expected time to reach b from x

$$h_x = h(x, b) \quad b \text{ fixed}$$

Lets write a recurrence

$$h_b = 0 \quad x \neq b \quad (*)$$

$$h_x = 1 + \sum_y h_y P_{xy}$$

How do we solve $(*)$?

lets think of h_x as a voltage V_x

$$V_b = 0 \quad V_x = 1 + \sum_y \frac{C_{xy}}{C_x} V_y$$

$$C_x V_x = C_x + \sum_y C_{xy} V_y$$

$$\underbrace{C_x V_x - \sum_y C_{xy} V_y}_{\text{Graph Laplacian}} = \underbrace{C_x}_{\text{residual current}}$$

Graph Laplacian residual current

$$L V = \begin{pmatrix} c_1 \\ \vdots \\ c_{n-1} \\ \delta \end{pmatrix}$$

$V_n = 0$

$$c = \sum c_i$$

$$b = V_n$$

by conservation of flow

$$\delta = c_n - c$$

Alg for hitting time

$$\text{solve } L V = \begin{pmatrix} c_1 \\ \vdots \\ c_{n-1} \\ c_n - c \end{pmatrix}$$

$V_n = 0$

return V_x

11
What about commute time?

$$a = v_1 \text{ \& \ } b = v_n$$

Solution 1

$$\text{solve } LV^b = \begin{pmatrix} c_n \\ \vdots \\ c_n - c \end{pmatrix} \quad LV^a = \begin{pmatrix} c_1 - c \\ \vdots \\ c_n \end{pmatrix}$$

$$h(1, n) = v_1^b - v_n^b$$

$$h(n, 1) = v_n^a - v_1^a$$

$$V = V^b - V^a$$

$$C(1, n) = (v_1^b - v_n^a) - (v_1^b - v_n^a)_n$$

Solution 2

$$L(V^b - V^a) = LV^b - LV^a = \begin{pmatrix} c_n \\ \vdots \\ c_n - c \end{pmatrix} - \begin{pmatrix} c_1 - c \\ \vdots \\ c_n \end{pmatrix} = \begin{pmatrix} c \\ \vdots \\ 0 \\ -c \end{pmatrix} = c \begin{pmatrix} 1 \\ \vdots \\ 0 \\ -1 \end{pmatrix}$$

solve $LV = \begin{pmatrix} 1 \\ 0 \\ \vdots \\ -1 \end{pmatrix}$

return $C(v_1, -v_n)$ but $(v_1, -v_n) = R_{1n}$

Thm $C(a, b) = R_{ab} \cdot C$