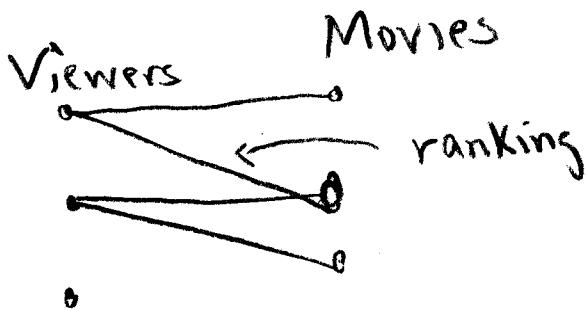


# Resistive Model of a Graph & Random Walks

15-859N  
9/9/13

Motivation: Making a recommendation  
(NETFLIX)



Question: Should we recommend  $M$  to  $V$ ?  
 $\text{Score}(V, M)$

Idea 1  $\text{Score}(V, M) = \frac{1}{\text{graph dist from } V \text{ to } M}$

$$W_{ij} = \frac{1}{\text{rank}_{ij}}$$

$$\text{Score}(V, M) = \frac{1}{\min_{M \in P} W(P)}$$

Idea 2  $W(P) = \min_{e \in P} (\text{rank}(e))$

$$\text{Score}(V, M) = \max_{V \in P_m} W(P)$$

Problem For 1) and 2) extra paths do not improve score

Idea 3  $\text{Score}(V, M) \equiv \text{Max flow from } V \text{ to } M.$

---

Problem Shorter paths do not improve score

---

Idea 4 View edges as conductors

$\text{Score}(V, M) = \text{effective conductance}$

Idea 5 Consider random walk from  $V$  to  $M$

$\text{Score}(V, M) = \text{hit.}(V, M) + \text{hit.}(M, V)$

$\text{hit.}(V, M) \equiv$  Expect length random walk from  $V, M$

We show 4) & 5) are related.

3

# Hypothesis:

effective conductance &

$$\text{Commute time} \equiv \text{hit}(v, m) + \text{hit}(m, v)$$


are better scores.

To do:

- 1) Give formal definitions.
- 2) Develop basic theory.
- 3) Give efficient algs.
- 4) Find apps.

# Resistance Theory

Ohms Law:

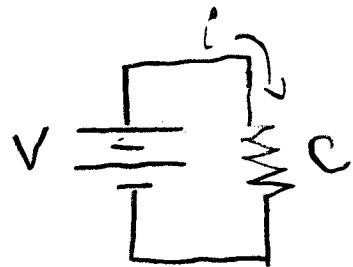

$C \equiv$  conductance

$R \equiv$  resistance


$V \equiv$  voltage

$i \equiv$  current

$$C = \frac{V}{R} \quad i = C \cdot V = \frac{V}{R}$$

Facts HW


Resistors in series

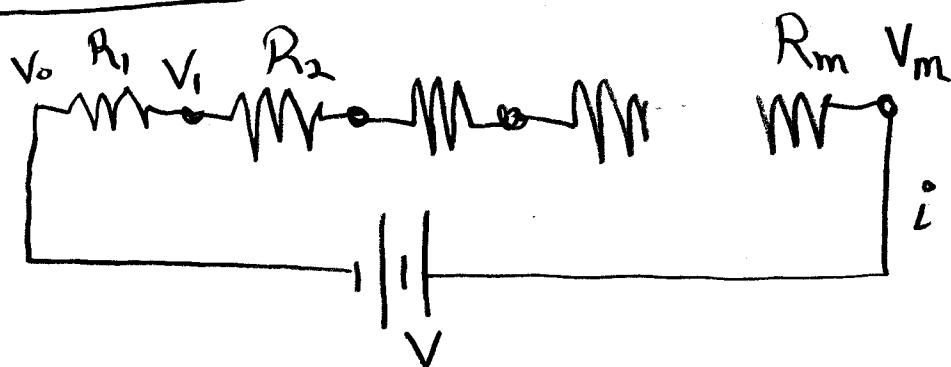

$$R = R_1 + \dots + R_m \quad C = \frac{1}{(\frac{1}{C_1} + \dots + \frac{1}{C_m})} = ?$$

$$\text{i.e. } i = \frac{V}{R}$$

## Conductors in Parallel

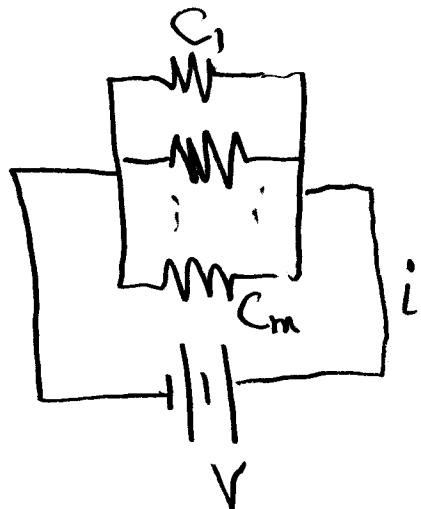


$$C = C_1 + \dots + C_m$$

$$\text{ie } i = V \cdot C$$

## Effective Resistance/Conductance

Let  $G$  be a network of resistors

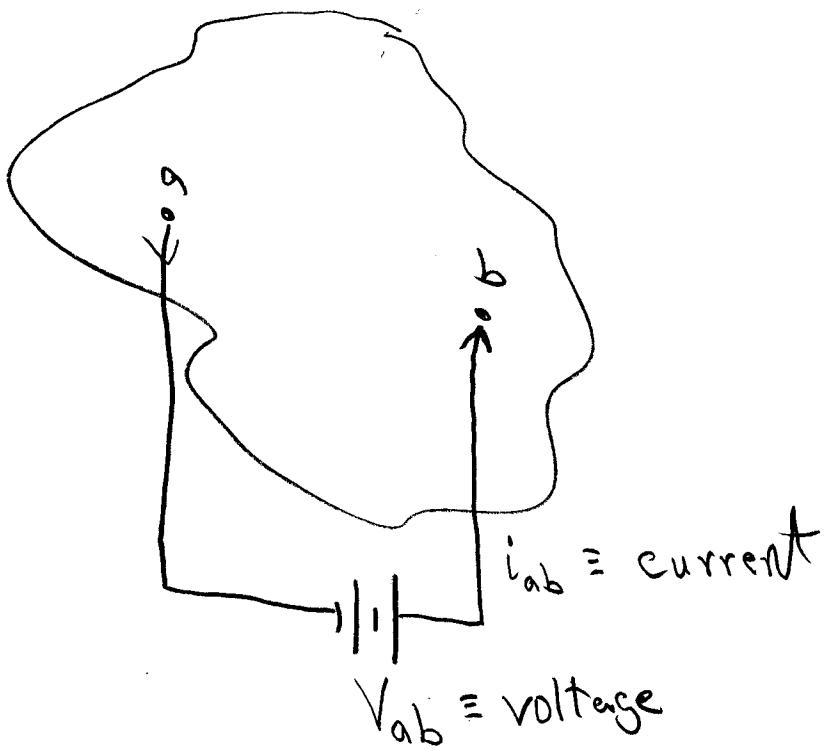


Def  $R_{ab} = V_{ab}/i_{ab}$      $C_{ab} = 1/R_{ab}$

# Computing effective resistance

Case<sup>o</sup>: Kirchhoff's Law ie flow in = flow out

an example

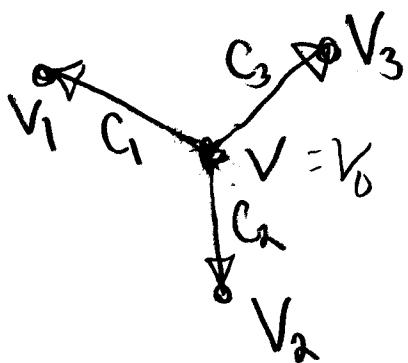

by Ohm's Law

$$i_1 = C_1(V - V_1)$$

$$i_2 = C_2(V - V_2)$$

$$i_3 = C_3(V - V_3)$$

$$\text{residual current} \equiv i_1 + i_2 + i_3$$

by Kirchhoff

$$i_1 + i_2 + i_3 = 0$$

$$C_1(V - V_1) + C_2(V - V_2) + C_3(V - V_3) = 0$$

$$(C_1 + C_2 + C_3)V = C_1V_1 + C_2V_2 + C_3V_3$$

$$C = C_1 + C_2 + C_3$$

$$CV = C_1 V_1 + C_2 V_2 + C_3 V_3$$

$$V = \frac{C_1}{C} V_1 + \frac{C_2}{C} V_2 + \frac{C_3}{C} V_3$$

$V$  is convex combination of  $V_1, V_2, V_3$

---

$$\text{residual current} = CV - C_1 V_1 - C_2 V_2 - C_3 V_3$$

The general case:

$$G = (V, E, C) \quad C: E \rightarrow \mathbb{R}^+$$

$$V = \{V_1, \dots, V_n\}$$

$$d(V_i) = \sum_{(i,j) \in E} C_{ij}$$

$$\text{Def: } A_{ii} = \begin{cases} C_{ii} & \text{if } (i,i) \in E \\ 0 & \text{o.w.} \end{cases}$$

$$\text{Laplacian}(G) = L(G) = L$$

$$L_{ij} = \begin{cases} d(v_i) & \text{if } i=j \\ -c_{ij} & \text{if } (i,j) \in E \\ 0 & \text{o.w.} \end{cases}$$

i.e.

$$L = D - A \quad \text{where } D = \begin{pmatrix} d(v_1) & & & \\ & \ddots & & 0 \\ & & \ddots & \\ 0 & & & d(v_n) \end{pmatrix}$$

Let  $V$  be a voltage setting of nodes

Note  $(LV)_i$  = residual current at  $v_i$

Inverse: We inject currents and get voltages.

The net injected must be zero!

Goal:  $R_{in}$

Method 1 solve  $b \begin{pmatrix} 0 \\ V_1 \\ \vdots \\ V_{n-1} \\ 1 \end{pmatrix} = \begin{pmatrix} i \\ 0 \\ \vdots \\ 0 \\ -i \end{pmatrix} \quad (*)$

$$i = V/R$$

$$N = V$$

$$R = V_i$$

return  $V_i$

$(*)$  is called a boundary valued prob.

In our case  $V_1$  &  $V_n$  are the bdary

$(V_1, \dots, V_n)$  is called harmonic

because  $V_i \in$  interior  $\Rightarrow$

$V_i$  is convex combination of neighbors

Maximum Principle If  $f$  is harmonic  
then min & max are on bdary

If  $V \in \text{interior}$  then  $\exists$  neig  $V_i \& V_j$  st

$$V_i \leq V \leq V_j$$


---

Uniqueness Principle If  $f \& g$  are harmonic

with same bdary values then  $f = g$

If  $f - g$  is harmonic with zero on bdary


$$\Rightarrow f - g \equiv 0 \Rightarrow f = g$$

Method 2

$$\text{solve } LV = \begin{pmatrix} 1 & & & \\ & 0 & & \\ & & \ddots & \\ & & & -1 \end{pmatrix} \text{ return } R_m = V_1 - V_n$$


Does  $V$  exist?

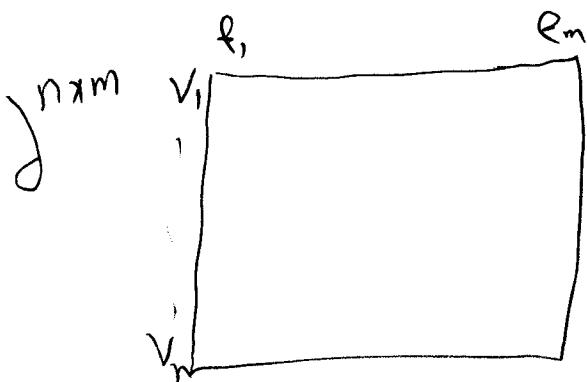Another way to view the Laplician  
Boundary Operator (Vertex-Edge Matrix)



Orient each edge:

	$e_1$	$e_2$	$e_3$
$v_1$	1	0	0
$v_2$	-1	-1	1
$v_3$	0	0	-1
$v_4$	0	1	0

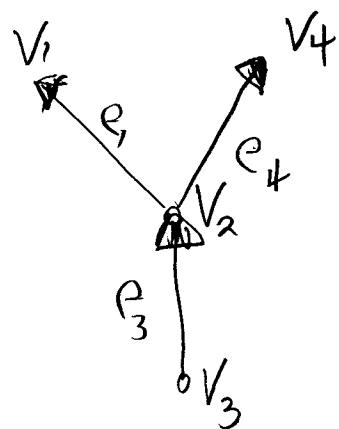

Let  $C_1 \dots C_m \equiv$  conductance of  $e_1 \dots e_m$

$$C = \begin{pmatrix} C_1 & 0 \\ 0 & \ddots \\ 0 & C_m \end{pmatrix}$$

Note  $\vec{J}^T V \equiv$  voltage drop across each edge  
 $C \vec{J}^T V \equiv$  current flow "

$\vec{J}^T C \vec{J}^T V \equiv$  residual current at each vertex

Thus  $L = \vec{J}^T C \vec{J}^T$


Assume  $G$  is a connected graph

$$\vec{x}^T C \vec{x} = (\vec{x})^T C \vec{x} = \sum C_{ij} (x_i - x_j)^2 \geq 0$$

$$\vec{x}^T L \vec{x} = 0 \text{ iff } \forall e_{ij} \quad (x_i - x_j)^2 = 0 \Rightarrow (x_i - x_j) = 0$$

$$\text{Ker}(L) = \langle \begin{pmatrix} 1 \\ 1 \\ \vdots \\ 1 \end{pmatrix} \rangle \quad \text{rank}(L) = n-1$$

# Current & Energy/Power Dissipation

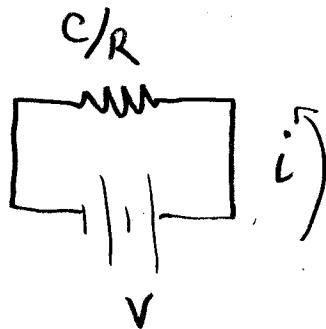

Newton

$$\begin{aligned}
 \text{Energy} &\equiv \text{Force} \cdot \text{speed} \\
 &\equiv \text{Volt} \cdot \text{current} \\
 &\equiv V \cdot i \\
 &\equiv CV^2 \\
 &\equiv i^2 R
 \end{aligned}$$

Network

$$E = \frac{1}{2} \sum_{x,y} i_{xy} (V_x - V_y)$$

$$\begin{aligned}
 V^T L V &= V^T J^T C J V = (\delta^T V)^T C (\delta^T V) \\
 &= \sum_{\substack{\text{Oriented} \\ (x,y) \in E}} C_{xy} (V_x - V_y)^2 = E
 \end{aligned}$$

## Two Types of Flow

Def: A flow  $f: E \rightarrow \mathbb{R}$  (oriented edges)

Def A potential flows =  $\{C^T V \mid V \in \mathbb{R}^n\} = P_G$

Def A circulations(flow) =  $\{f \in \mathbb{R}^n \mid \delta f = 0\} = C_G$

---

Assume  $G$  is connected &  $T$  spanning tree

Claim  $C_G$  is a subspace &  $\dim(C_G) = m - n + 1$

$m = \# \text{edges}$ :

1) Subspaces easy

2)  $E \setminus T \equiv \text{non tree edges of } G$

$$|E \setminus T| = m - n + 1$$

3) Claim any flow on  $E \setminus T$  can be extended to  $C_G$  on  $G$ . (HW)

4)  $f, g \in C_G$  and  $f \setminus T = g \setminus T$  then  $f = g$ .

Claim  $f_c \in C_G$  &  $g_p \in P_G$  thus  $f_c^T R g_p = 0$

$$\text{when } R = \begin{pmatrix} R_1 & 0 \\ 0 & R_m \end{pmatrix}$$

Pf  $\exists v \text{ st } g_p = C \bar{\partial} V$

$$f_c^T R g_p = f_c^T R C \bar{\partial} V = f_c^T \bar{\partial} V = (\bar{\partial} f_c)^T V = 0^T V = 0$$

note  $R C = I$

Thus  $C_G, P_G$  spans  $\mathbb{R}^m$  (all flows)

$$\text{if } \forall f \in \mathbb{R}^m \exists! f_c \& f_p \text{ st } f = f_c + f_p$$

Def  $f_a = \sum_{a \neq b} f_{ab}$

Def  $f$  is a unit flow from  $a$  to  $b$  if:

1)  $f$  is a flow

2)  $f_a = f_b = 1$

3)  $f_x = 0$  for  $x \neq a, b$ .

## Thomson's Principle

- 1)  $f$  is unit Potential flow from a tab
- 2)  $g$  is any flow from a tab.

then  $f^T R f \leq g^T R g$

---

$R_f$

We know that  $g = f + f_c$   $f_c \equiv$  circulation

$$\begin{aligned} g^T R g &= (f + f_c)^T R (f + f_c) = f^T R f + 2 \cancel{f_c^T R f} + \cancel{f_c^T R f_c} \\ &= f^T R f + f_c^T R f \geq f^T R f \end{aligned}$$


---

note

Def on Thm Effective resistance from a tab

$$ER_{ab} = f_p^T R f_p$$

$f_p \equiv$  unit potential flow from a tab.

# Rayleigh's Monotonicity Law

$$\bar{R} \geq R \text{ then } \bar{ER}_{ab} \geq ER_{ab}$$

Pf  $f \equiv$  unit potential flow in  $G_R$   
 $g \equiv$  in  $G_{\bar{R}}$

$$\bar{ER}_{ab} = g^T \bar{R} g = \sum_{e \in G} g_e^2 \bar{R}_e$$

$$\geq \sum_{e \in G} g_e^2 R_e$$

$$\geq \sum_{e \in G} f_e^2 R_e \quad (\text{Thomson})$$

$$= f_e^T R f_e = ER_{ab}$$

Hw) Show that  $R_{ab}$  is a metric space

ie 1)  $R_{ab} \geq 0$

2)  $R_{ab} = 0$  iff  $a = b$

3)  $R_{ab} = R_{ba}$

4)  $R_{ac} \leq R_{ab} + R_{bc}$