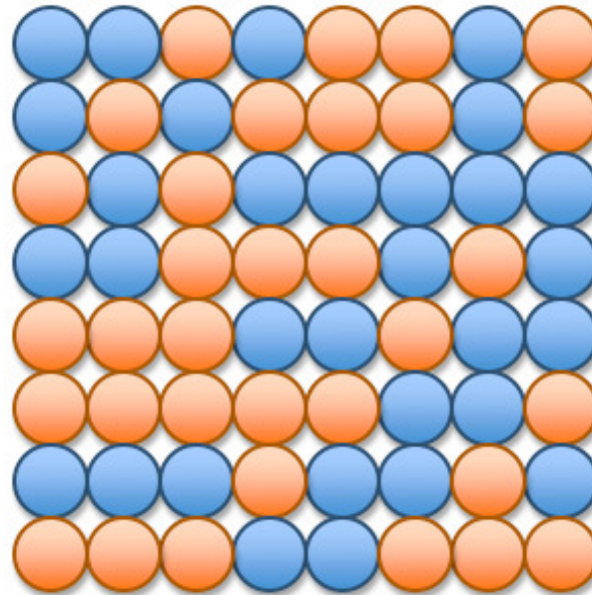




UNIT 8A

Computer Organization: Boolean Logic, Computational Circuits

Boolean Logic & Truth Tables

- Computer circuitry works based on Boolean logic: operations on true (1) and false (0) values.

A	B	$A \wedge B$ (A AND B) (conjunction)	$A \vee B$ (A OR B) (disjunction)
0	0	0 ✓	0
0	1	0 ✓	1
1	0	0 ✓	1
1	1	1 ✓	1

A	$\neg A$ (NOT A) (negation)
0	1
1	0

01
10
—
11 ✓

Exercise

- Write the truth table for

$$E = \boxed{A \wedge B \wedge C} \quad \checkmark$$

$$\neg A \vee B$$

A	B	
0	0	1
0	1	1
1	0	0
1	1	1

$$\neg A \vee B \wedge A$$


do this

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	1	1	0
1	1	1	1


Gates

- A gate is an electronic device that implements a logical function. (Images from Wikipedia)


- Circuit diagram:

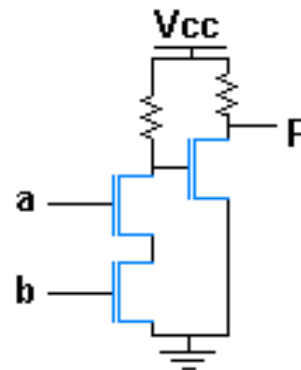

NMOS
AND gate



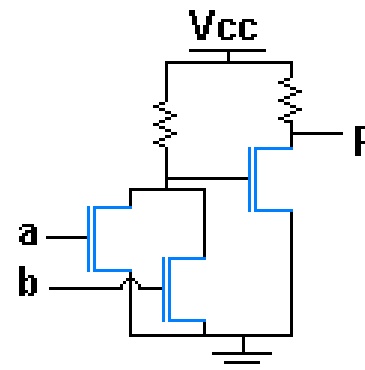


NMOS
OR gate

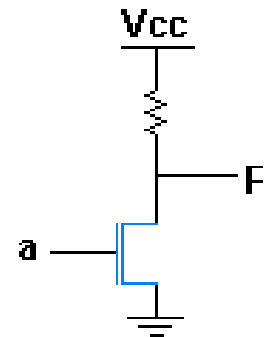

NMOS
NOT gate


- Abstract
Diagram:

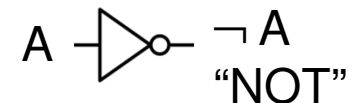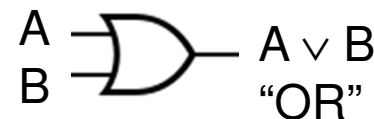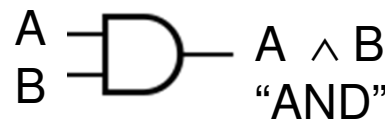


Exercise

- Draw the following using $\rightarrow$ $\begin{matrix} A \\ B \end{matrix} \rightarrow \text{AND} \rightarrow A \wedge B$ $\begin{matrix} A \\ B \end{matrix} \rightarrow \text{OR} \rightarrow A \vee B$ $A \rightarrow \text{NOT} \rightarrow \neg A$

$$(A \wedge B) \wedge C$$

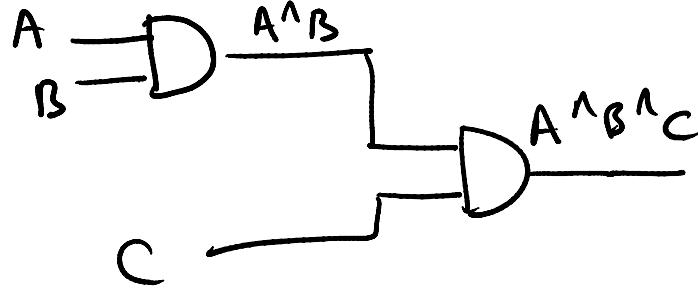

$$\neg A \vee B$$

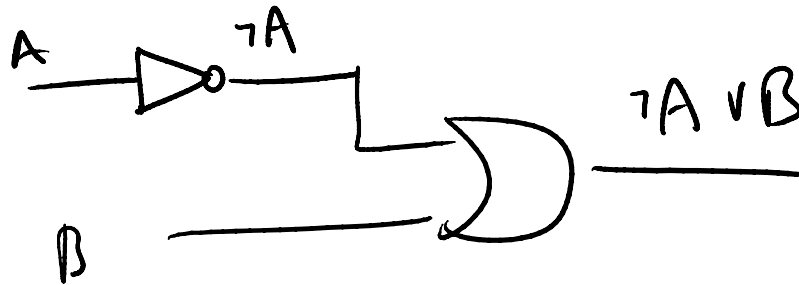

$$\neg A \vee B \wedge A$$

Properties (Similar to $\times$ and $+$)

- Commutative: $a \wedge b = b \wedge a$ $a \vee b = b \vee a$
- Associative: $a \wedge b \wedge c = (a \wedge b) \wedge c = a \wedge (b \wedge c)$
 $a \vee b \vee c = (a \vee b) \vee c = a \vee (b \vee c)$
- Distributive: $a \wedge (b \vee c) = (a \wedge b) \vee (a \wedge c)$
 $a \vee (b \wedge c) = (a \vee b) \wedge (a \vee c)$ Not true for
+ and $\times$
- Identity: $a \wedge 1 = a$ $a \vee 0 = a$
- Dominance: $a \wedge 0 = 0$ $a \vee 1 = 1$
- Idempotence: $a \wedge a = a$ $a \vee a = a$
- Complementation: $a \wedge \neg a = 0$ $a \vee \neg a = 1$
- Double Negation: $\neg \neg a = a$


DeMorgan's Law

Nand: $\neg(A \wedge B) = \neg A \overset{\text{or}}{\vee} \neg B$

if **not** ($x > 15$ **and** $x < 110$) then

is logically equivalent to

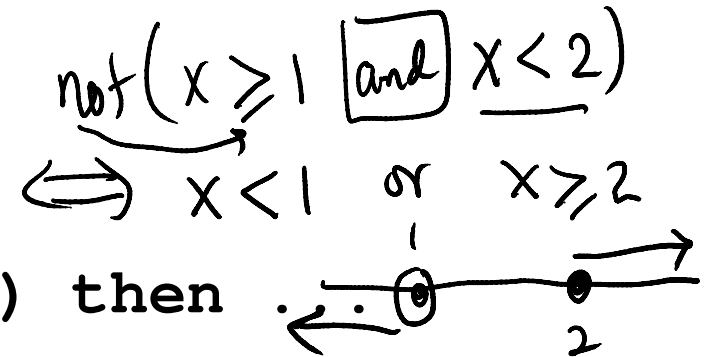if (**not** $x > 15$) **or** (**not** $x < 110$) then ...




Nor: $\neg(A \vee B) = \neg A \wedge \neg B$

if **not** ($x < 15$ **or** $x > 110$) then ...

is logically equivalent to

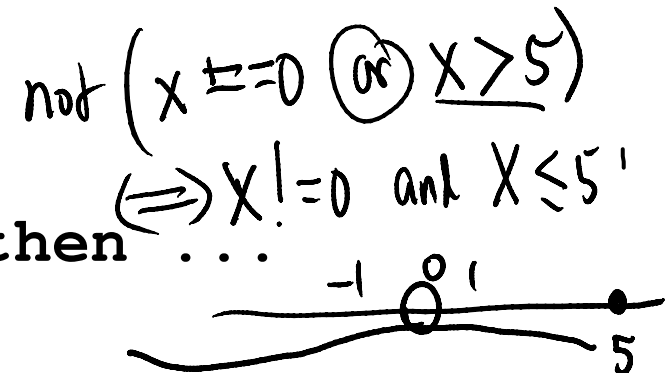if (**not** $x < 15$) **and** (**not** $x > 110$) then ...



Simplify/rewrite


$$\underline{A \wedge A = A}$$

$$\bullet \quad \underline{(A \wedge A) \wedge A = A} \longrightarrow (A) \wedge A \rightarrow A$$

$$\bullet \quad A \wedge (B \wedge \neg B) \Rightarrow A \wedge 0 \Rightarrow 0$$

$$\bullet \quad \neg ((A \vee B) \wedge C) \Rightarrow \neg (A \vee B) \vee \neg C$$
$$\Rightarrow \neg A \wedge \neg B \vee \neg C$$

Equivalence

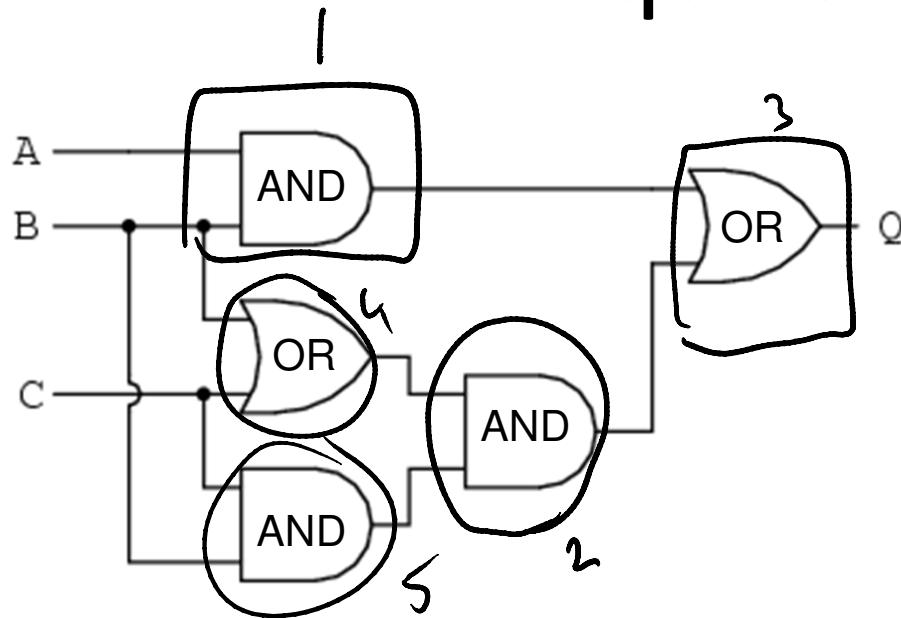

$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$


Handwritten annotations below the equation:

- Arrow from 1 to $A \wedge B$
- Arrow from 3 to $\vee$
- Arrow from 4 to $(B \vee C)$
- Arrow from 2 to $(C \wedge B)$
- Arrow from 5 to $(C \wedge B)$


A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	✓
0	1	1	✓
1	0	0	✓
1	0	1	
1	1	0	
1	1	1	

http://www.allaboutcircuits.com/vol_4/chpt_7/6.html

Equivalence

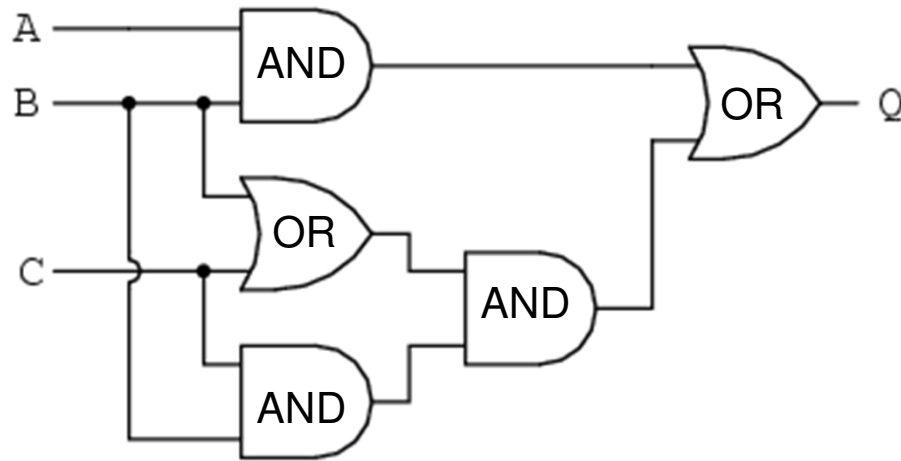
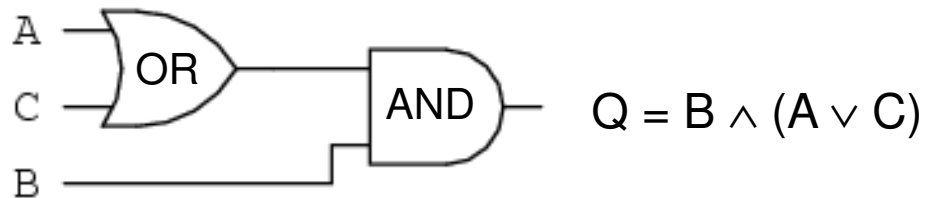
$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$



$$Q = B \wedge (A \vee C)$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

http://www.allaboutcircuits.com/vol_4/chpt_7/6.html

Show equivalence

- $Q = \boxed{(A \wedge B)} \vee ((\boxed{B \vee C}) \wedge \boxed{C \wedge B})$
- $Q = B \wedge (A \vee C)$

$$P \vee Q \wedge P \vee R$$

$$(A \wedge B) \vee Q$$

$$A \vee Q \wedge B \vee Q$$


$$A \vee (B \vee C) \wedge \boxed{B \vee (B \vee C)}$$

~~A~~ ~~A~~


More gates

A	B	A nand B	A nor B	A xor B
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	0

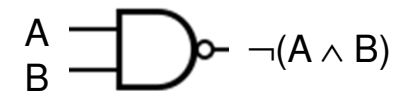
- nand (“not and”): $A \text{ nand } B = \neg(A \wedge B)$



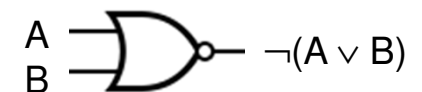- nor (“not or”): $A \text{ nor } B = \neg(A \vee B)$



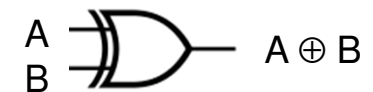
- xor (“exclusive or”):
 $A \text{ xor } B = (A \text{ and not } B) \text{ or } (B \text{ and not } A)$




Exercise

- $(\neg A \wedge \neg B)$ using a NAND gate

Gates Are Built From Transistors

 

Transistor (switch)

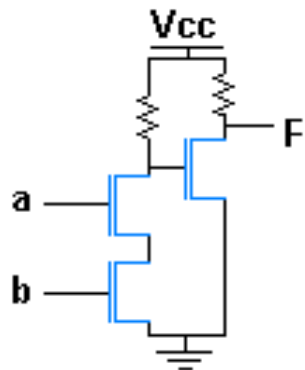

NMOS
AND gate



Every spot where a red line crosses a green line is a transistor. →

