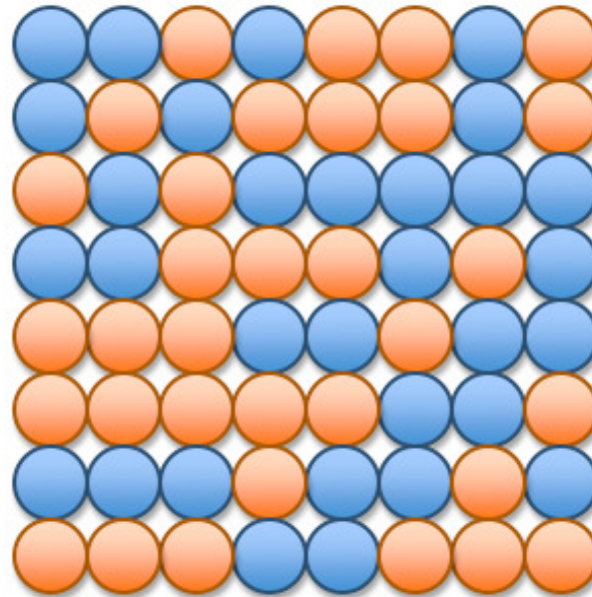




UNIT 8B


Computer Organization: Levels of Abstraction

Announcements

- Midsemester grades will be assigned this weekend
- Ps7 is due ~~Friday~~ ^{Wed} March ~~22~~ ²⁰ in class
- Pa7 will be assigned shortly (due after break)

Abstraction

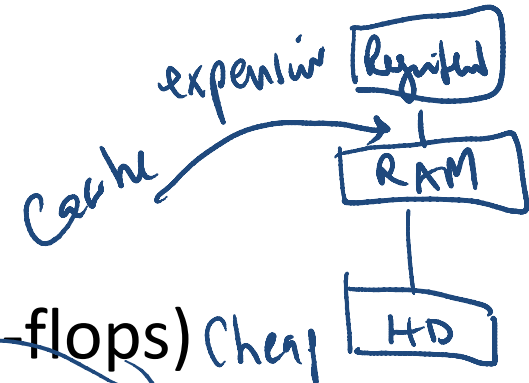
- We can use layers of abstraction to hide details of the computer design.
- We can work in any layer, not needing to know how the lower layers work or how the current layer fits into the larger system.
 - > transistors
 - > gates
 - > circuits (adders, multiplexors, flip-flops)
 - > central processing units (ALU, registers, control)
 - > computer




Central Processing Unit (CPU)

- A CPU contains:

- Arithmetic Logic Unit to perform computation
- Registers to hold information
 - Instruction register (current instruction being executed)
 - Program counter (to hold location of next instruction in memory)
 - Accumulator (to hold computation result from ALU)
 - Data register(s) (to hold other important data for future use)
- Control unit to regulate flow of information and operations that are performed at each instruction step

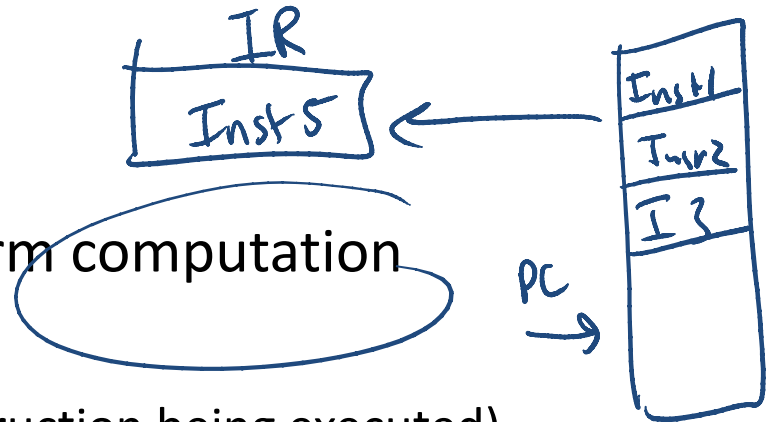


A sample CPU

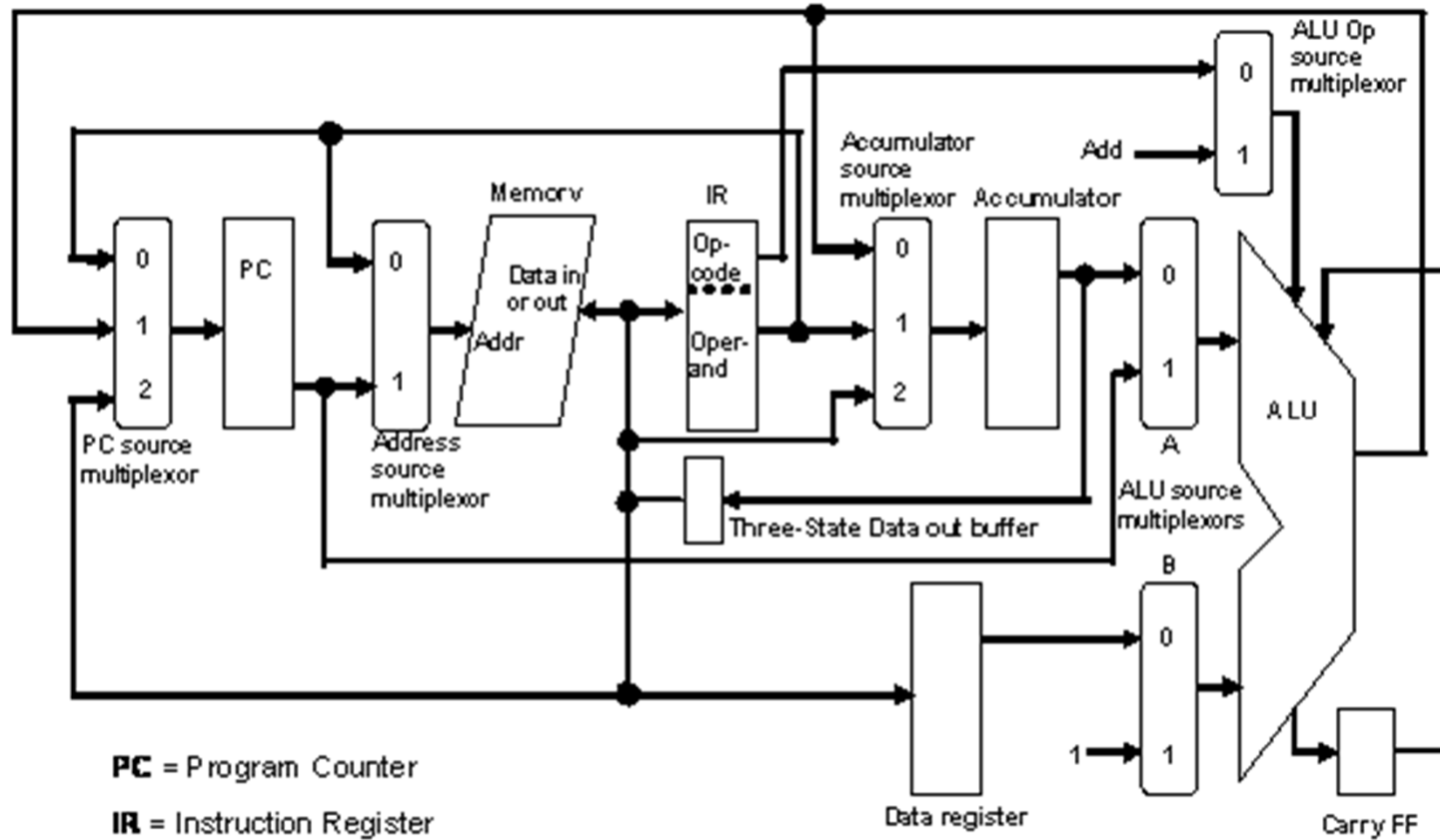




<http://cpuville.com/main.htm>

Computer

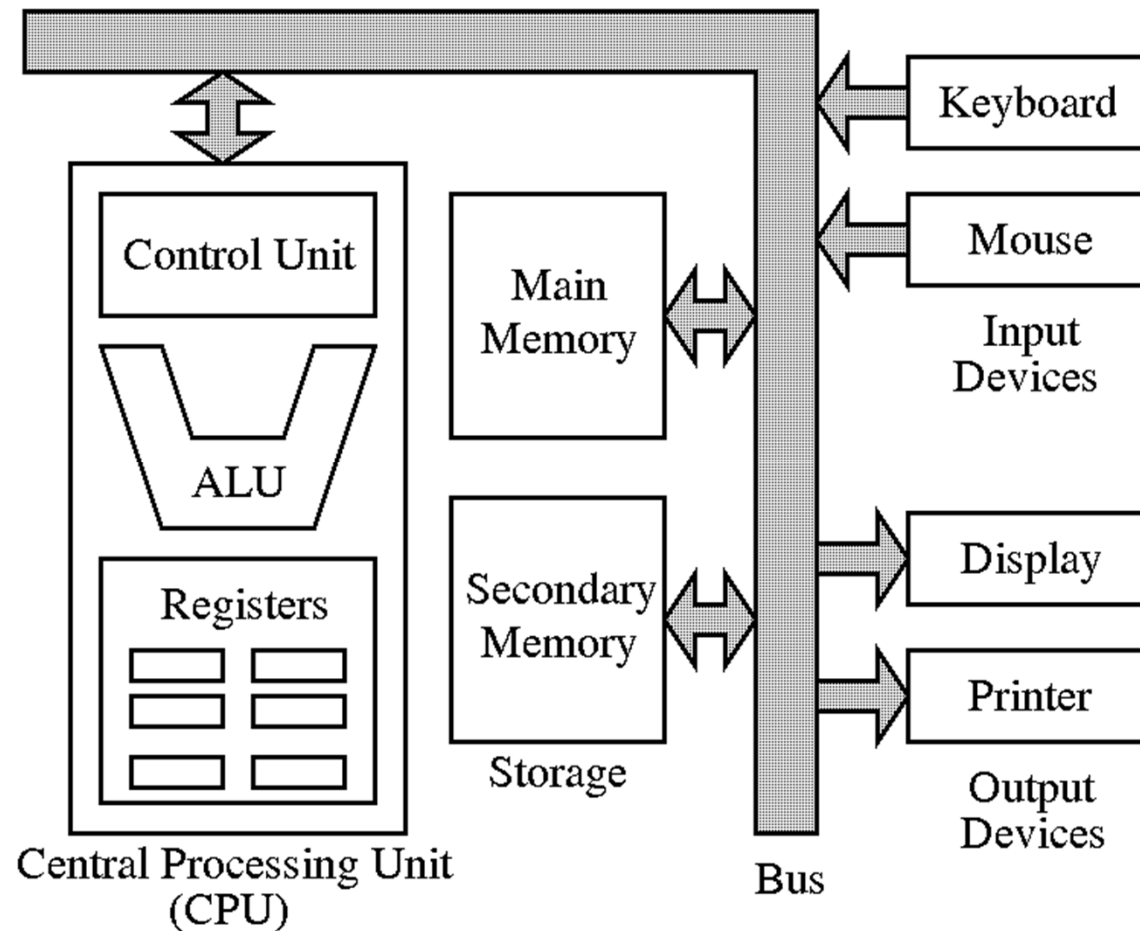

<http://cse.iitkgp.ac.in/pds/notes/intro.html>



To Gates

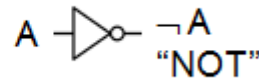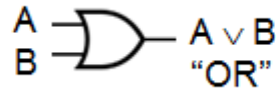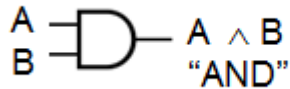

Properties (Similar to $\times$ and $+$)

- Commutative: $a \wedge b = b \wedge a$ $a \vee b = b \vee a$
- Associative: $a \wedge b \wedge c = (a \wedge b) \wedge c = a \wedge (b \wedge c)$
 $a \vee b \vee c = (a \vee b) \vee c = a \vee (b \vee c)$
- Distributive: $a \wedge (b \vee c) = (a \wedge b) \vee (a \wedge c)$
 $a \vee (b \wedge c) = (a \vee b) \wedge (a \vee c)$ Not true for + and $\times$
- Identity: $a \wedge 1 = a$ $a \vee 0 = a$
- Dominance: $a \wedge 0 = 0$ $a \vee 1 = 1$
- Idempotence: $a \wedge a = a$ $a \vee a = a$
- Complementation: $a \wedge \neg a = 0$ $a \vee \neg a = 1$
- Double Negation: $\neg \neg a = a$

equivalence

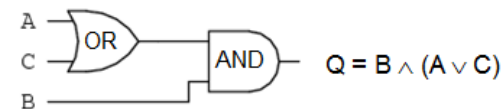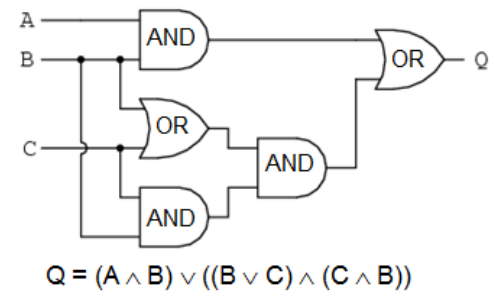

More gates




A	B	A nand B	A nor B	A xor B
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	0

A	B	A or B
0	0	0
0	1	1
1	0	1
1	1	1








$$\begin{array}{r}
 A \quad 0 \quad 0 \quad 1 \quad 1 \\
 B \quad 0 \quad 1 \quad 0 \quad 1 \\
 \hline
 \quad 0 \quad 1 \quad 1 \quad 0
 \end{array}$$

$$A \oplus B \rightarrow \text{Sum}$$

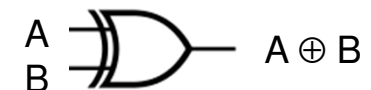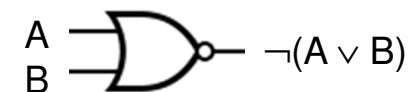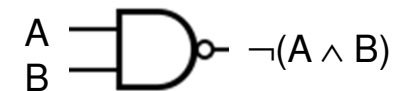
- nand (“not and”): $A \text{ nand } B = \text{not } (A \text{ and } B)$
- nor (“not or”): $A \text{ nor } B = \text{not } (A \text{ or } B)$
- xor (“exclusive or”):
 $A \text{ xor } B = (A \text{ and not } B) \text{ or } (B \text{ and not } A)$



All Gates

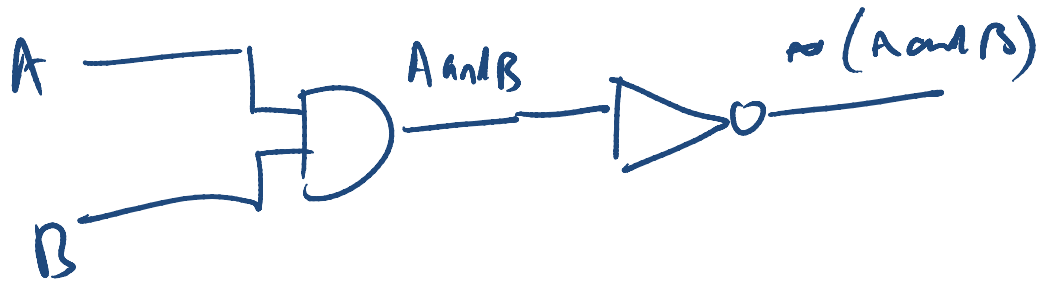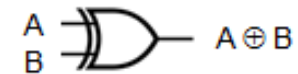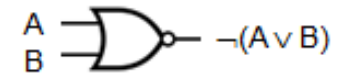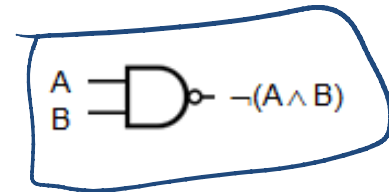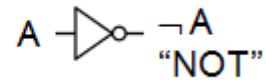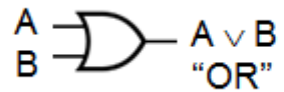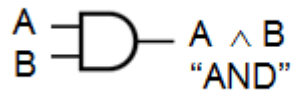
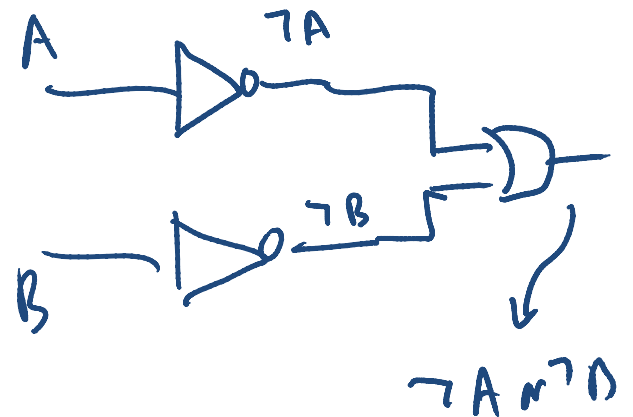
$$\neg(A \text{ and } B) = \neg A \text{ or } \neg B$$




Adding Binary Numbers

$$A = \begin{array}{r} 1111\ 101 \\ 1010\ 1101 \end{array} \checkmark$$

$$B = 0101\ 1101 \checkmark$$

overflow $\rightarrow$ $\boxed{1}0000101\boxed{0}$

$$A \oplus B$$

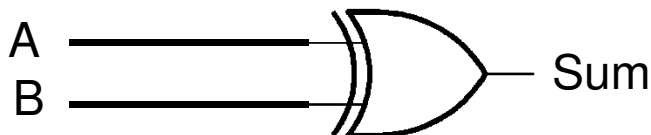


base-2 addition

$$\begin{array}{r} \text{Carry} \\ \textcircled{1} \\ 2 \overline{) 3} \\ \underline{2} \\ \textcircled{1} \\ \text{Sum bit} \end{array}$$


Adding Binary Numbers

$$\text{Sum} = A \oplus B$$


$$\text{Carry} = A \text{ and } B$$

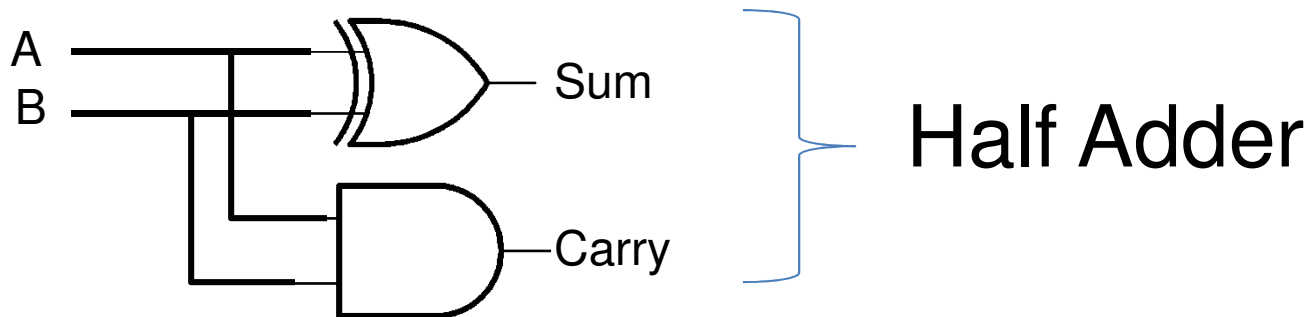

A Full Adder

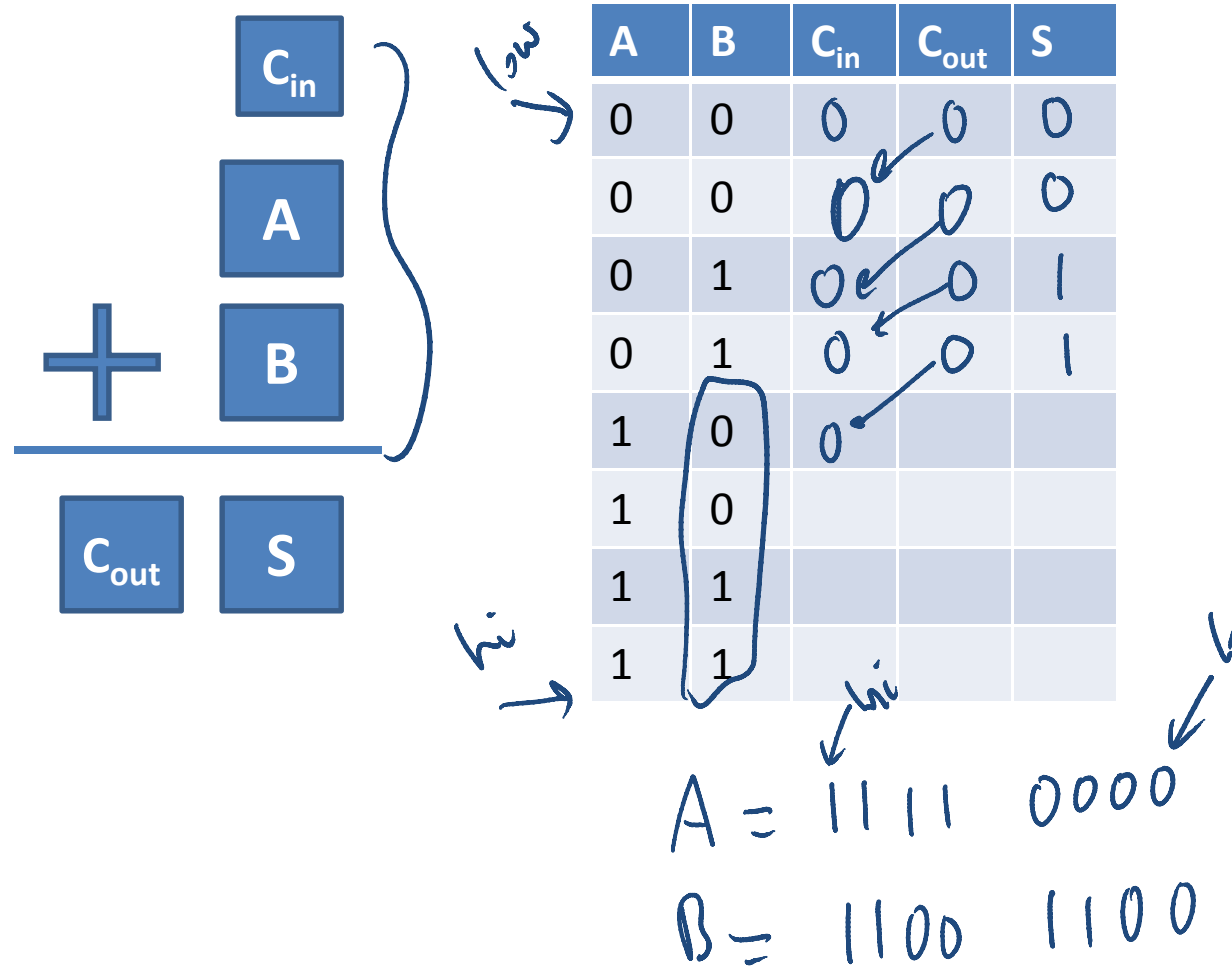

A Full Adder

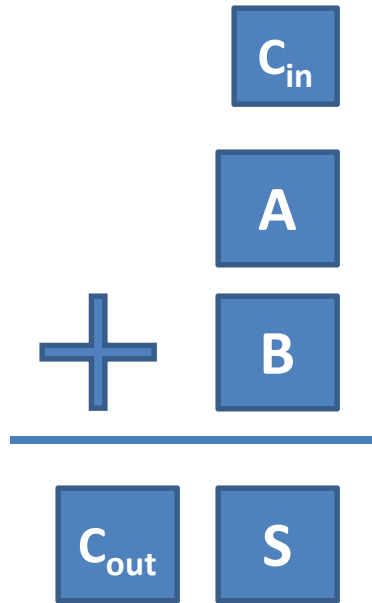


A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$


$$C_{out} = ((A \oplus B) \wedge C_{in}) \vee (A \wedge B)$$

Full Adder (FA)

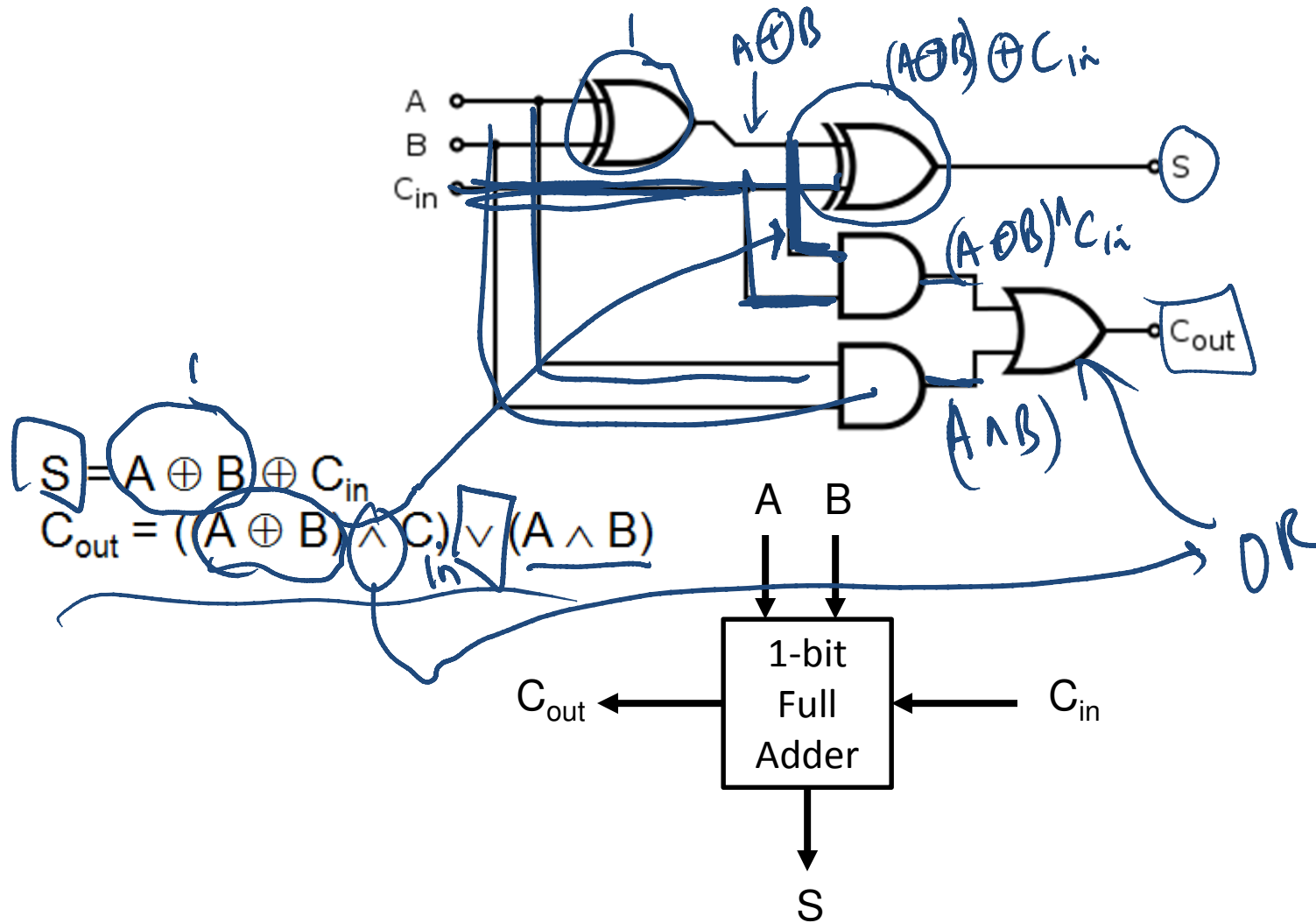


Another Full Adder (FA)






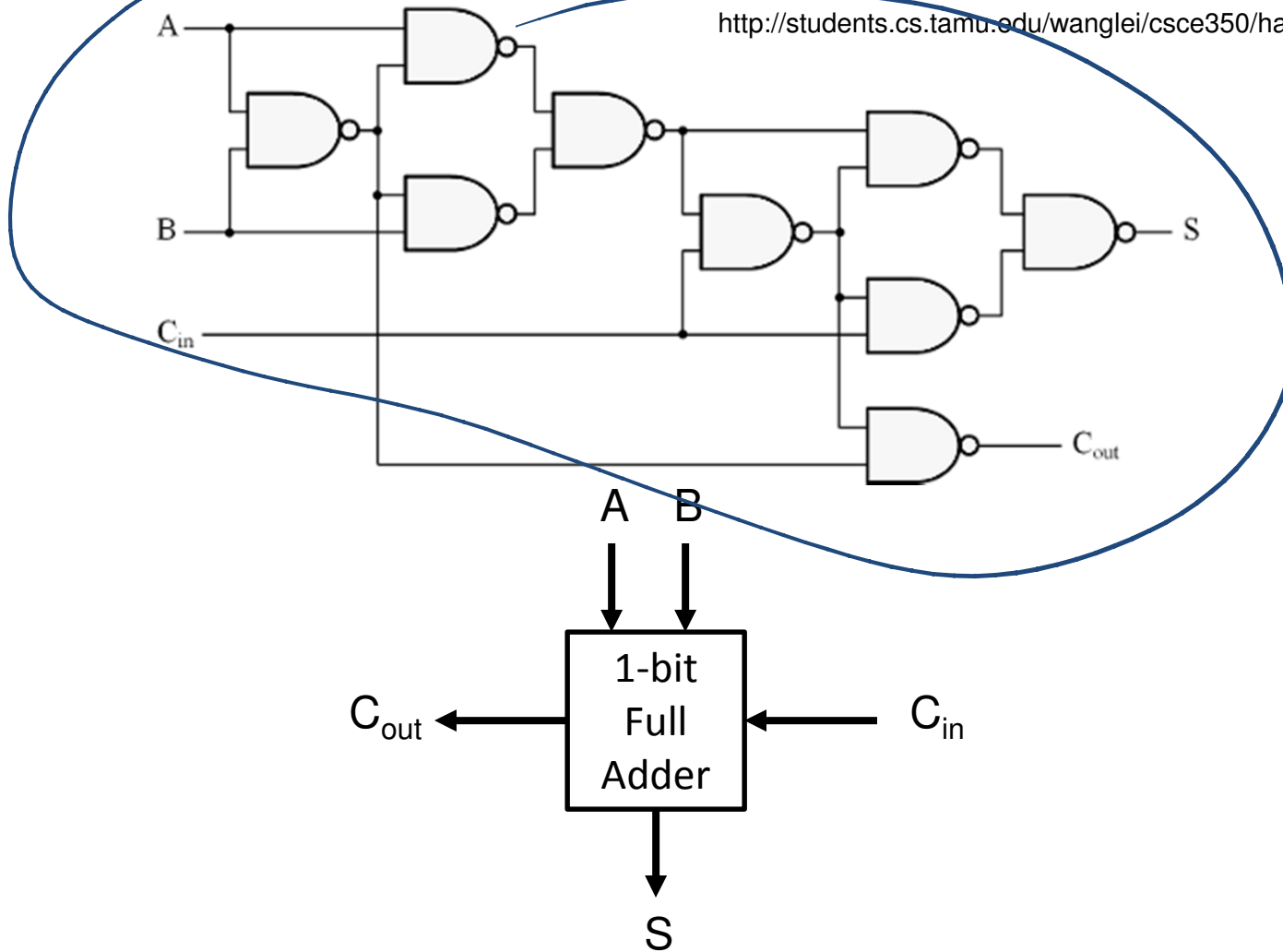
<http://students.cs.tamu.edu/wanglei/csce350/handout/lab6.html>




8-bit Full Adder

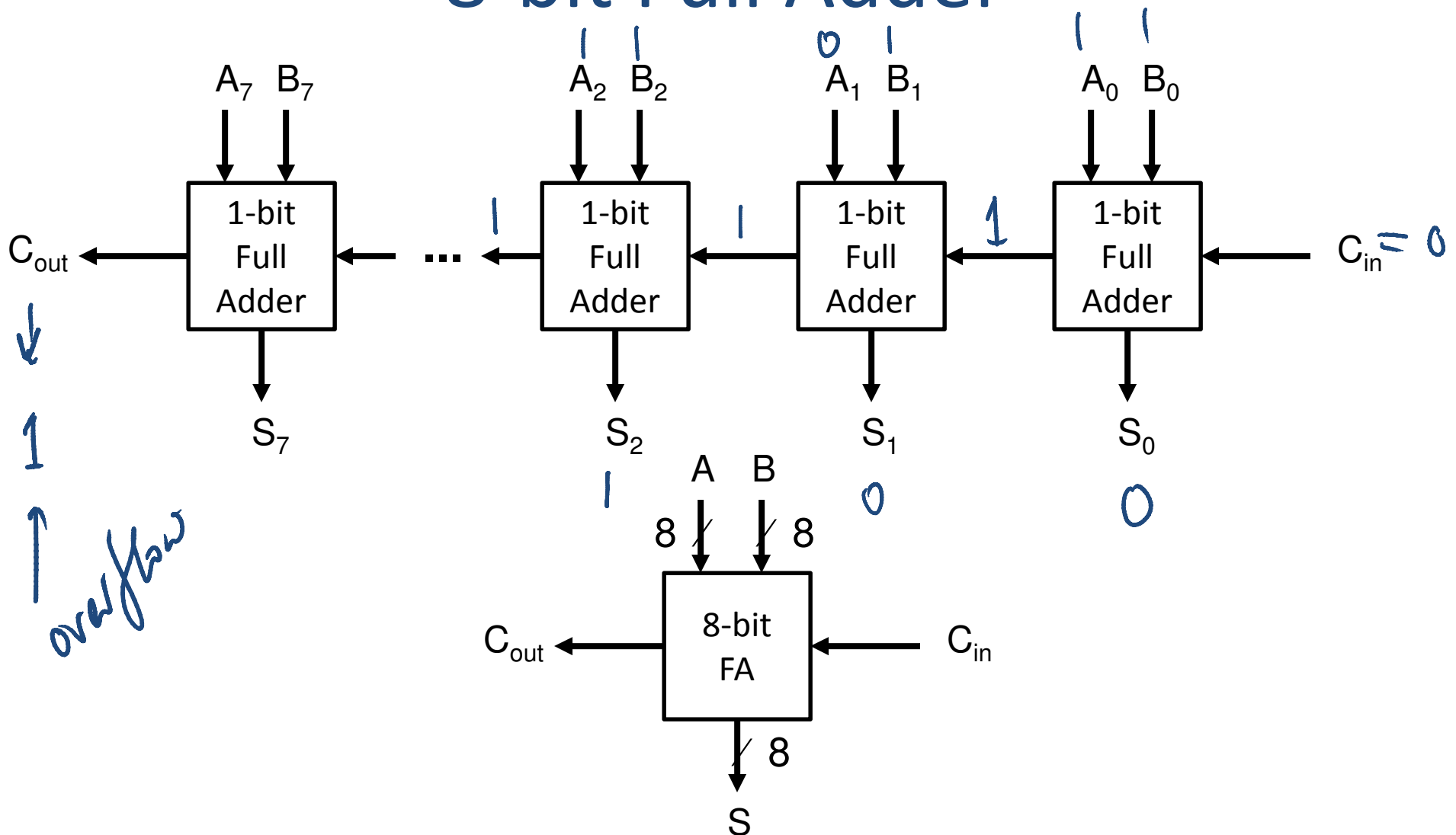







Exercise

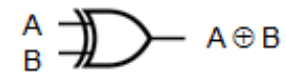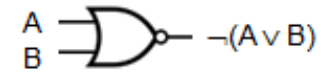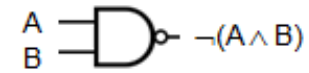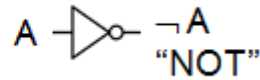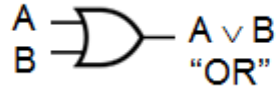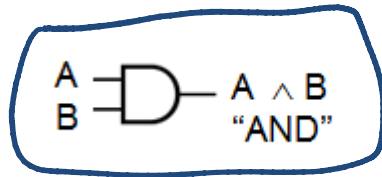


- Convert expressions to circuit

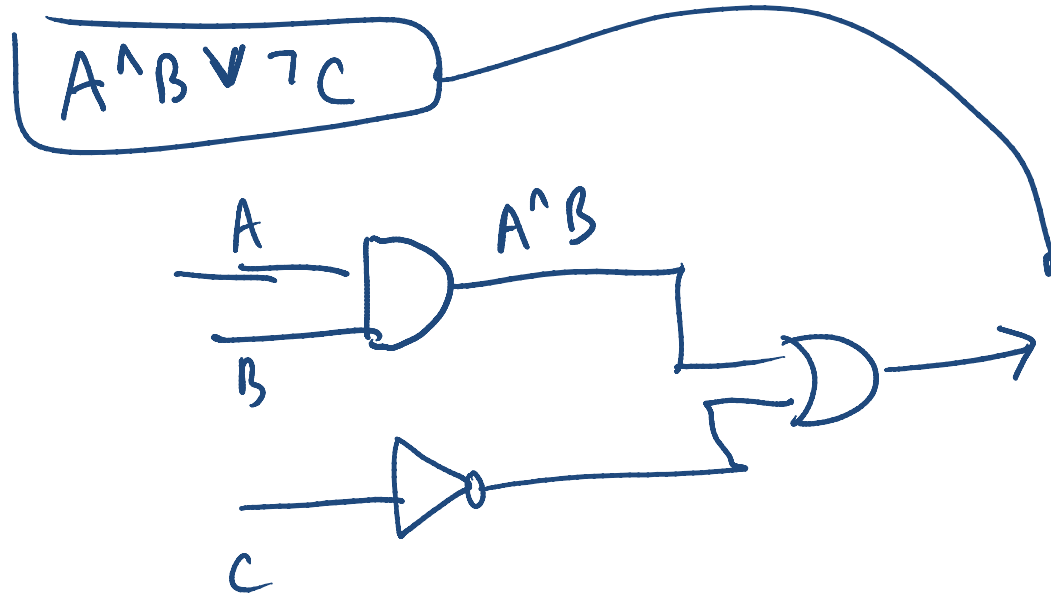

Exercise

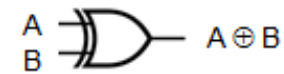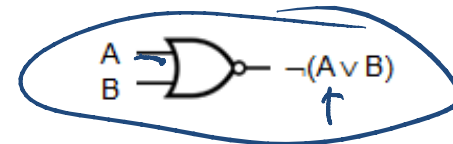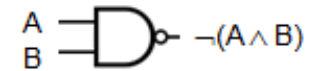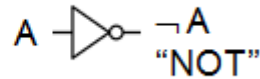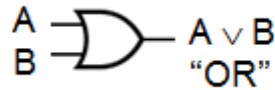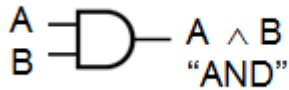


- Convert circuit to expressions

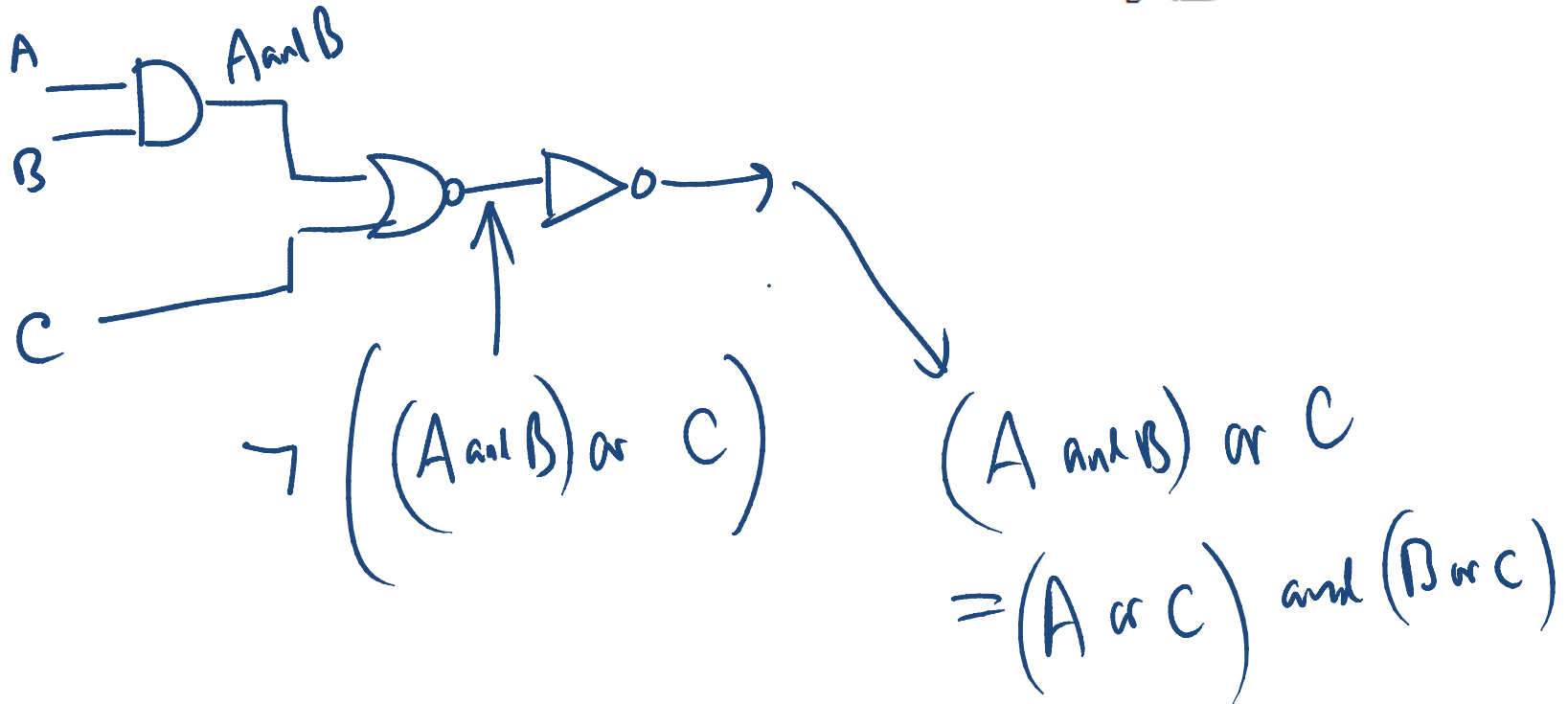

exercise

- Designing a control system

1,0 ↓ A	1,0 ↓ B	1,0 ↓ C	output
1	1	0	1 → $A \cdot B \cdot \bar{C}$
0	0	1	0
1	1	1	1 → $A \cdot B \cdot C$
0	1	1	1 → $\bar{A} \cdot B \cdot C$

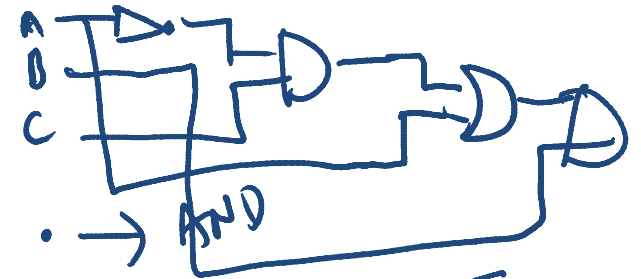

$$A \cdot B \cdot (\bar{C} + C) + \bar{A} \cdot B \cdot C$$

$$A \cdot B \cdot 1 + \bar{A} \cdot B \cdot C$$

$$B \cdot (A + \bar{A} \cdot C)$$

Simplified

$$E = A \cdot B \cdot \bar{C} + A \cdot B \cdot C + \bar{A} \cdot B \cdot C$$

From Design to circuits

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1