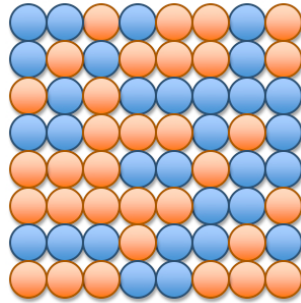





UNIT 8B

Computer Organization: Levels of Abstraction

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

1

A Full Adder

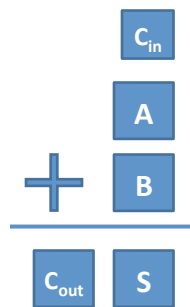


A	B	C_{in}	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

2

A Full Adder

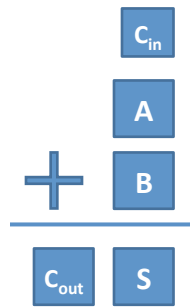

A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in} \text{ (the odd parity function!)}$$

$$C_{out} = ((A \oplus B) \wedge C_{in}) \vee (A \wedge B)$$


15110 Principles of Computing,
Carnegie Mellon University - CORTINA

3

Full Adder (FA)

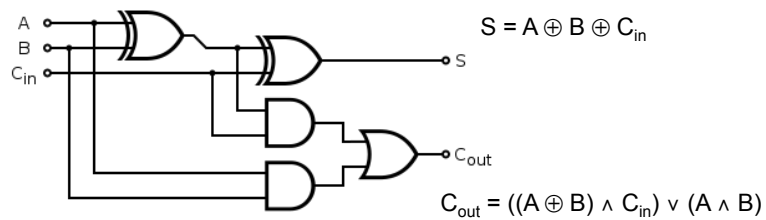


Abstractly:

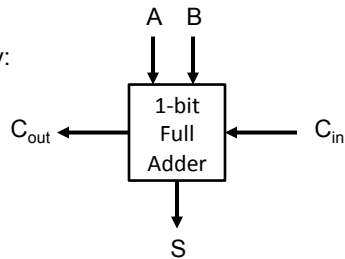


15110 Principles of Computing,
Carnegie Mellon University - CORTINA

4

Another Full Adder (FA)

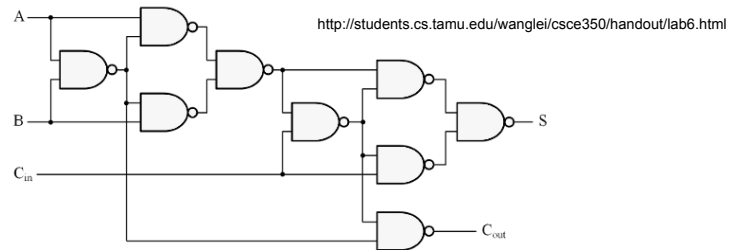


Still the same abstractly:

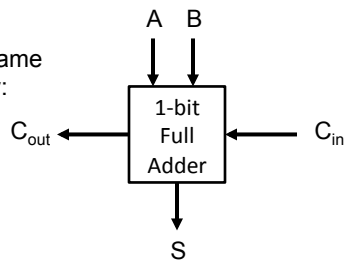

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

5

8-bit Full Adder

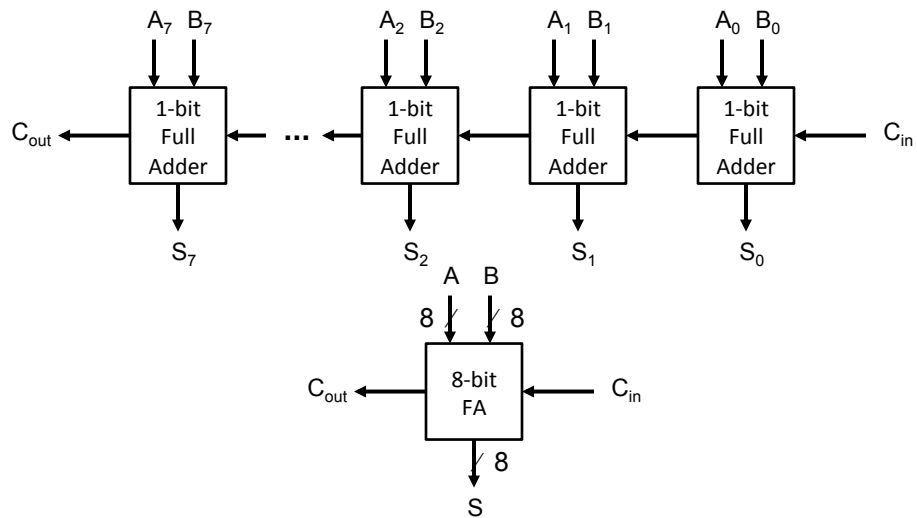


15110 Principles of Computing,
Carnegie Mellon University - CORTINA

6

Multiplexer (MUX)

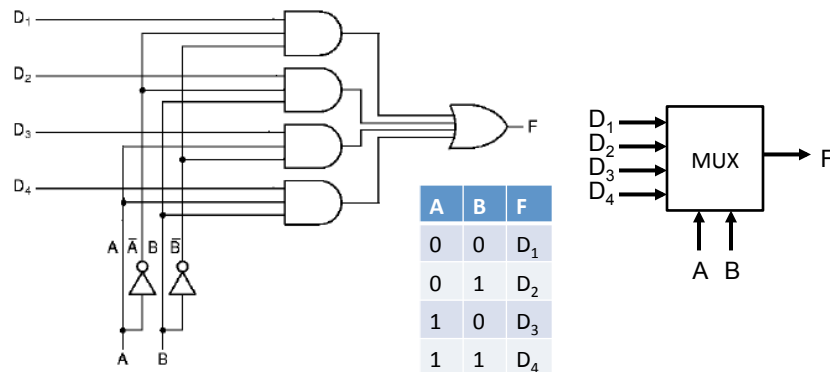- A multiplexer chooses between a set of inputs.




<http://www.cise.ufl.edu/~mssz/CompOrg/CDAintro.html>

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

7

Arithmetic Logic Unit (ALU)

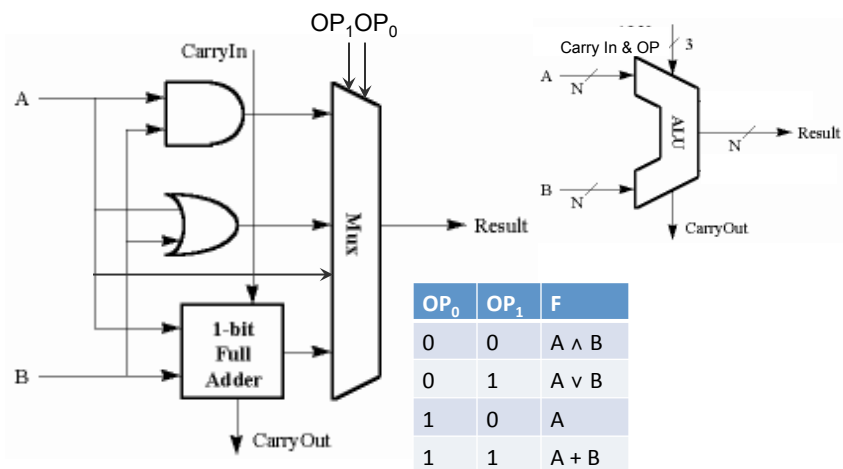



<http://cs-alb-pc3.massey.ac.nz/notes/59304/I4.html>

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

8

Flip Flop

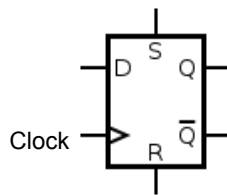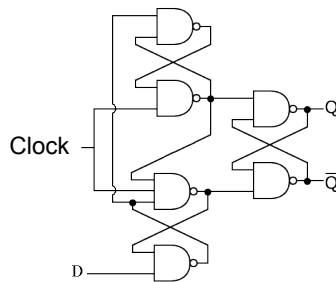- A flip flop is a sequential circuit that is able to maintain (save) a state.
 - Example: D (Data) Flip-Flop – sets output Q to input D when clock turns on. (Images from Wikipedia)





S=Set Q to 1,
R=Reset Q to 0

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

9

Registers

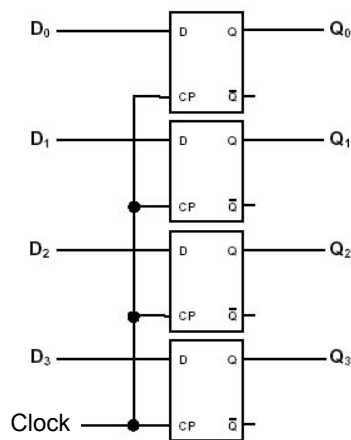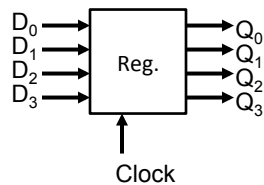- A memory register is just a set of edge-triggered flip-flops. Registers are triggered by a clock signal.



<http://cpuville.com/register.htm>


15110 Principles of Computing,
Carnegie Mellon University - CORTINA

10

Central Processing Unit (CPU)


- A CPU contains:
 - Arithmetic Logic Unit to perform computation
 - Instruction register (current instruction being executed)
 - Program counter (to hold location of next instruction in memory)
 - Accumulator (to hold computation result from ALU)
 - Data register(s) (to hold other important data for future use)
 - Registers to hold information
 - Instruction register (current instruction being executed)
 - Program counter (to hold location of next instruction in memory)
 - Accumulator (to hold computation result from ALU)
 - Data register(s) (to hold other important data for future use)
 - Control unit to regulate flow of information and operations that are performed at each instruction step

A sample CPU

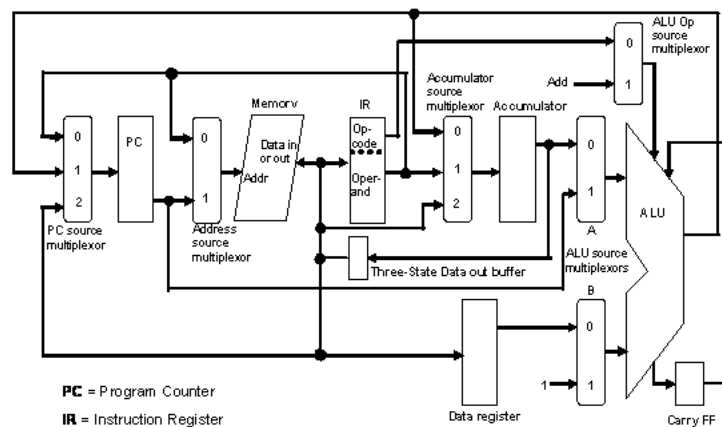

<http://cpuville.com/main.htm>

Computer

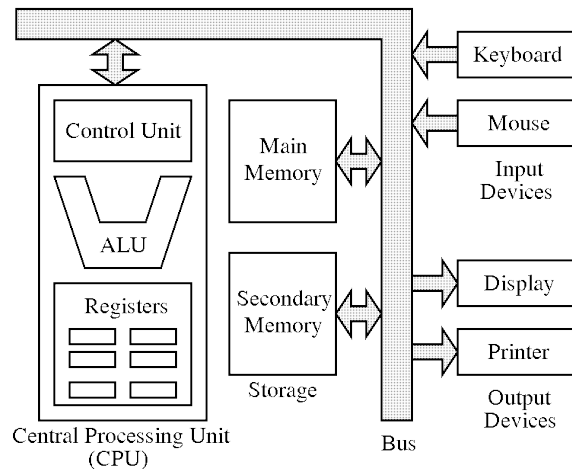

<http://cse.iitkgp.ac.in/pds/notes/intro.html>

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

13

Abstraction

- We can use layers of abstraction to hide details of the computer design.
- We can work in any layer, not needing to know how the lower layers work or how the current layer fits into the larger system.
 - > transistors
 - > gates
 - > circuits (adders, multiplexors, flip-flops)
 - > central processing units (ALU, registers, control)
 - > computer

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

14

Programming a Machine

- All instructions for a program are stored in computer memory in binary, just like data.
- A program is needed that translates human readable instructions (e.g. in Python) into binary instructions (“machine language”).
 - An interpreter is a program that translates one instruction at a time into machine language to be executed by the computer.
 - A compiler is a program that translates an entire program into machine language which is then executed by the computer.

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

15

von Neumann Architecture

- Most computers follow the **fetch-decode-execute** cycle introduced by John von Neumann.
 - Fetch next instruction from memory.
 - Decode instruction and get any data it needs (possibly from memory).
 - Execute instruction with data and store results (possibly into memory).
 - Repeat.

15110 Principles of Computing,
Carnegie Mellon University - CORTINA

16